
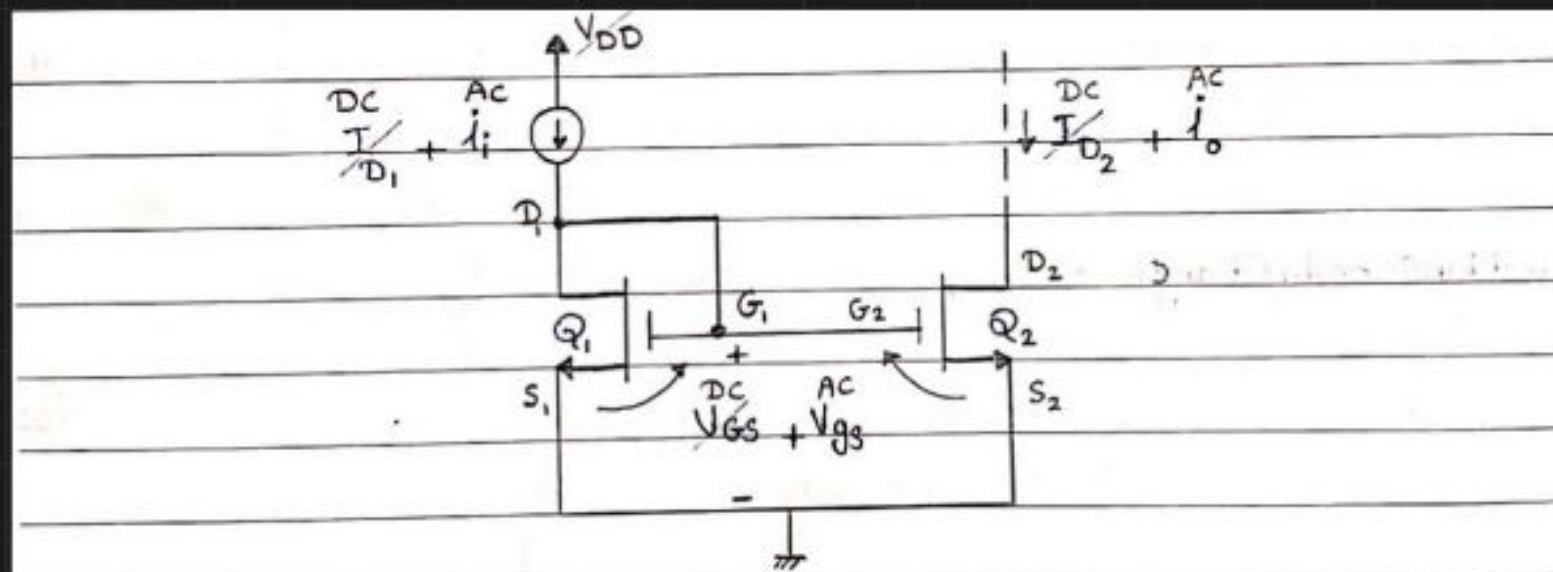


## ★ AC analysis:

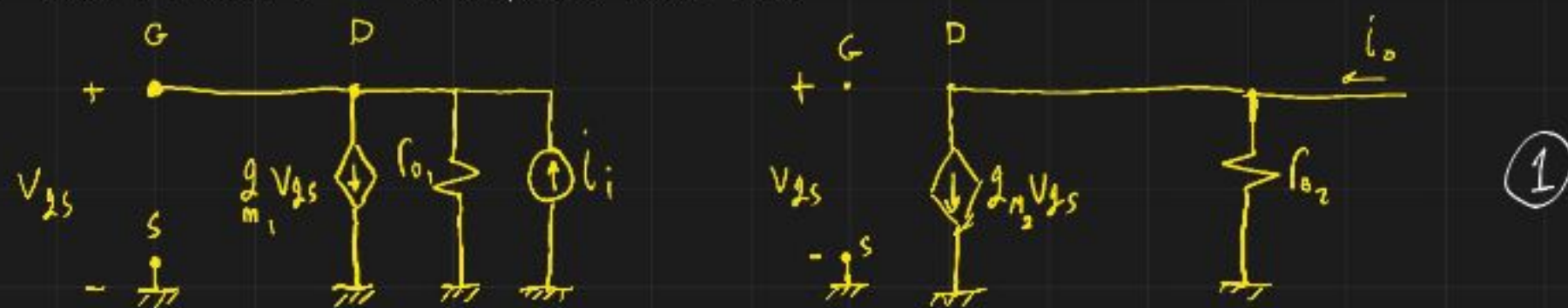

→ Small signal model for the current mirror:



→ Current amplifier small signal model:



• the goal is to map (2) to (1)

$$\rightarrow i_i = \frac{V_{gs}}{r_{o1}} + g_{m1} V_{gs} = V_{gs} \left( g_{m1} + \frac{1}{r_{o1}} \right)$$

$$\rightarrow R_{in} = \frac{V_{gs}}{i_i} = \frac{1}{g_{m1} + 1/r_{o1}} \rightarrow \therefore \frac{1}{R_{in}} = \frac{1}{r_{o1}} + g_{m1} \rightarrow \therefore R_{in} = r_{o1} \parallel \frac{1}{g_{m1}}$$

→  $R_o$ : independent C.s → o.c, independent V.s → s.c

$$\therefore R_o = r_{o2}$$

→  $A_{is}$ : Connect S.C to the o.p →  $r_{o2} = 0 \rightarrow R_o = 0$

$$A_{is} = \frac{i_o}{i_i} \quad \therefore i_o = g_{m2} V_{gs}$$

$$\therefore V_{gs} = i_i R_{in}$$

$$\therefore A_{is} = \frac{g_{m2} V_{gs}}{V_{gs}/R_{in}} \rightarrow \therefore A_{is} = g_{m2} R_{in}$$





$$A_{is} = g_{m2} R_{in} \quad \therefore R_{in} = \frac{1}{\frac{1}{r_{o1}} + g_{m1}} = \frac{1}{g_{m1}} \cdot \frac{1}{1 + \frac{1}{g_{m1} r_{o1}}}$$

$$\therefore A_{is} = \frac{g_{m2}}{g_{m1}} \cdot \frac{1}{1 + \frac{1}{g_{m1} r_{o1}}} \rightarrow (5)$$

$$\therefore g_m = \sqrt{I_D} \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)} = \frac{2 I_D}{V_{ov}} \quad \therefore g_m \propto I_D$$

$$\therefore \frac{g_{m2}}{g_{m1}} = \frac{I_{D2}}{I_{D1}} \rightarrow (6)$$

Sub from (6) in (5)


$$A_{is} = \frac{I_{D2}}{I_{D1}} \cdot \frac{1}{1 + \frac{1}{g_{m1} r_{o1}}}$$

$\therefore$  from saturation eqn  $I_D \propto \frac{W}{L}$

$$A_{is} = \frac{(W/L)_2}{(W/L)_1} \cdot \frac{1}{1 + \frac{1}{g_{m1} r_{o1}}}$$

## 2. Common source amplifier with Current Source Load

Ex (8.3) Page (555)

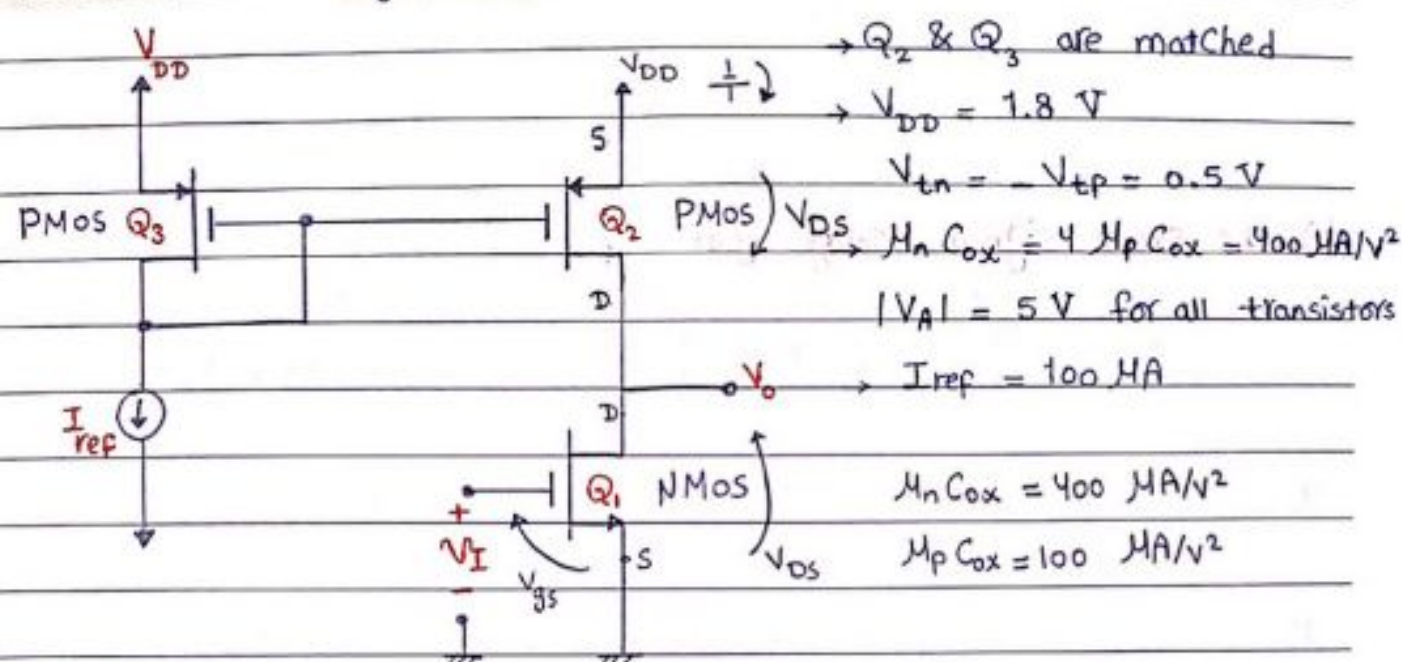

find:

- DC Component of  $V_I$  &  $\frac{W}{L}$  for all transistors at  $|V_{ov}| = 0.2V$ .
- the small signal voltage gain  $A_v$ .
- allowable range of signal swing at the o/p for almost linear operation.

$$a) V_I = V_{I_{DC}} + V_{I_{AC}} \quad , \quad V_{I_{DC}} = V_{gs_{DC}} = V_{ov} + V_t = 0.2 + 0.5$$

$$\therefore V_{I_{DC}} = 0.7V$$

$$Q_1) I_{D1} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L}\right)_1 (V_{ov})^2$$

$$\therefore 100 = \frac{1}{2} (400) \left(\frac{W}{L}\right)_1 (0.2)^2$$

$$\therefore \left(\frac{W}{L}\right)_1 = 12.5$$

$$Q_{2,3}) I_{D2} = \frac{1}{2} (\mu_p C_{ox}) \left(\frac{W}{L}\right)_2 (V_{ov})^2$$

$$\therefore 100 = \frac{1}{2} (100) \left(\frac{W}{L}\right)_2 (0.2)^2$$

$$\therefore \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = 50$$

b)

$$A_v = \frac{V_o}{V_{gs}} = \frac{-g_{m1} V_{gs} (r_{o1} // r_{o2})}{V_{gs}}$$

$$\therefore A_v = -g_{m1} (r_{o1} // r_{o2})$$

$$\rightarrow g_{m1} = \frac{2I_{D1}}{V_{ov1}} = \frac{2(100\mu)}{0,2}$$

$$\therefore g_{m1} = 1 \text{ mA/V}$$

$$\rightarrow r_{o1} = \frac{V_A}{I_{D1}} = \frac{5}{100\mu}$$

$$\therefore r_{o1} = 50 \text{ k}\Omega$$

$$\rightarrow r_{o2} = \frac{V_A}{I_{D2}} = \frac{5}{100\mu}$$

$$\therefore r_{o2} = 50 \text{ k}\Omega$$

$$\therefore r_{o1} // r_{o2} = 25 \text{ k}\Omega$$

$$\therefore A_v = -(1)(25) = -25$$



c) signal swings around the DC value

$$Q_1) V_{DS1} > V_{ov1}$$

$$\therefore V_{DS1} = V_o \quad \therefore V_{DS_{min}} = V_{ov1} \rightarrow \therefore V_{o_{min}} = 0,2 \text{ V}$$

$$\therefore V_o > 0,2 \rightarrow \textcircled{1}$$

$$Q_2) V_{DS2} \leq V_{ov2}$$

$$\therefore V_o = V_{DD} + V_{DS2} \rightarrow \therefore V_o - V_{DD} \leq V_{ov2}$$

$$\therefore V_o \leq V_{DD} + V_{ov2}$$

$$\therefore V_o \leq 1,8 + (-0,2)$$

$$\therefore V_o \leq 1,6 \text{ V} \rightarrow \textcircled{2}$$

$$\therefore 0,2 \leq V_o \leq 1,6$$

