
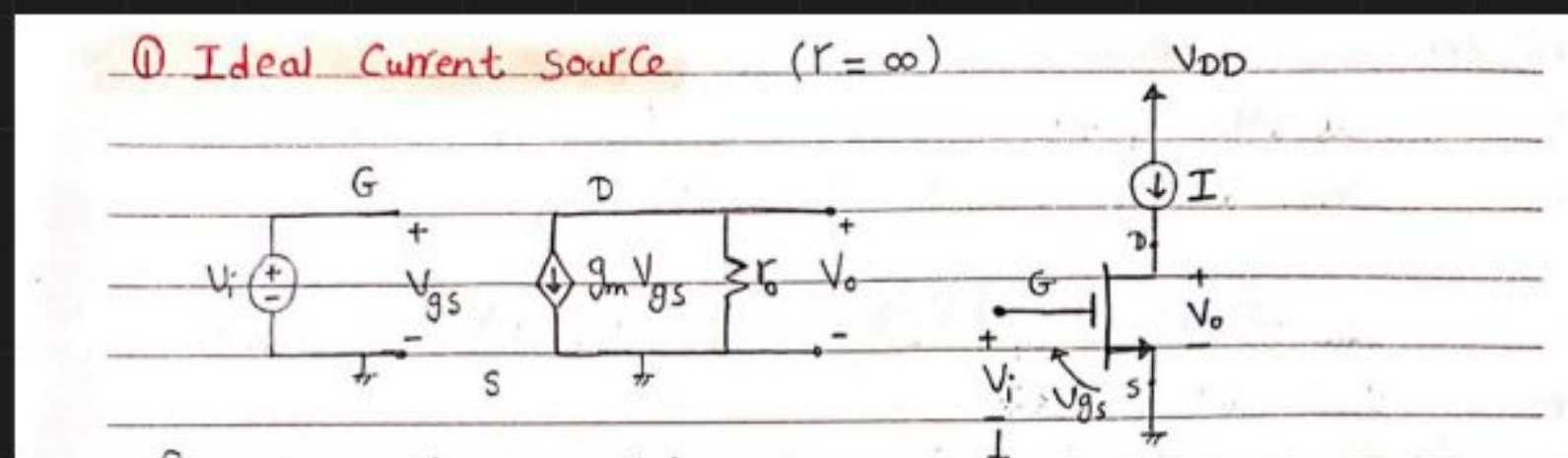
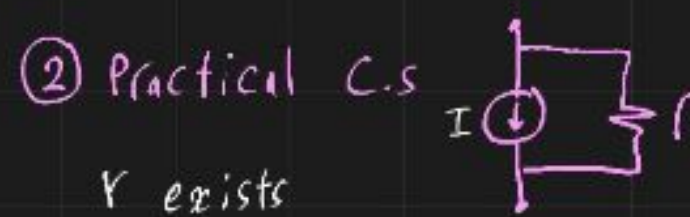


• active loads in common source amp. can be current source or Mosfet.


• current source model:

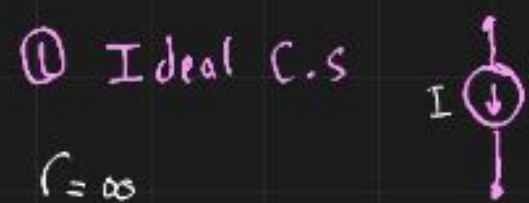

$$1) R_{in} = \frac{V_i}{I_i} = \frac{V_i}{0} = \infty$$

$$2) R_{out} \text{ at } V_i = 0 \rightarrow V_{gs} = 0 \rightarrow R_{out} = r_o$$
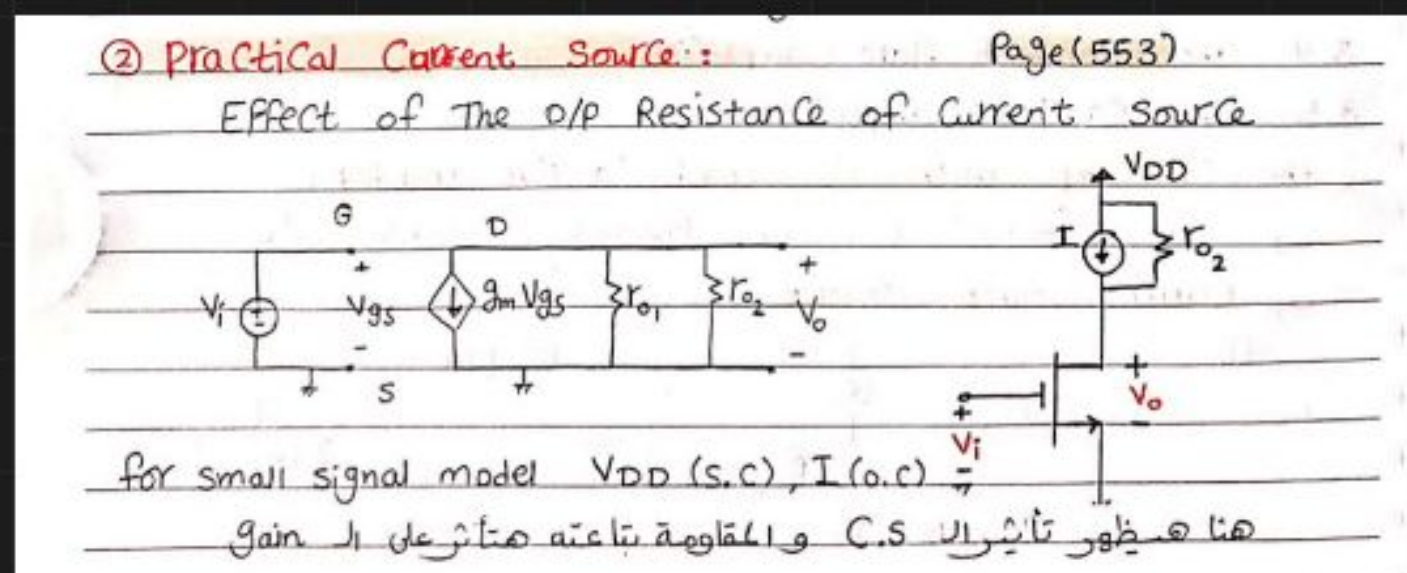
$$3) A_{v_o} = \frac{V_o}{V_i} = \frac{-g_m V_{gs} r_o}{V_{gs}} \rightarrow A_{v_o} = -g_m r_o \quad \text{"intrinsic gain"}$$




$$1) R_{in} = \infty$$

$$2) R_{out} = r_{o1} \parallel r_{o2}$$

$$3) A_v = -g_m (r_{o1} \parallel r_{o2}) \quad , \text{ if } r_{o1} = r_{o2} \rightarrow A_v = \frac{1}{2} A_{v_o}$$

Common Gate amplifier:

8.4 Common gate amplifier

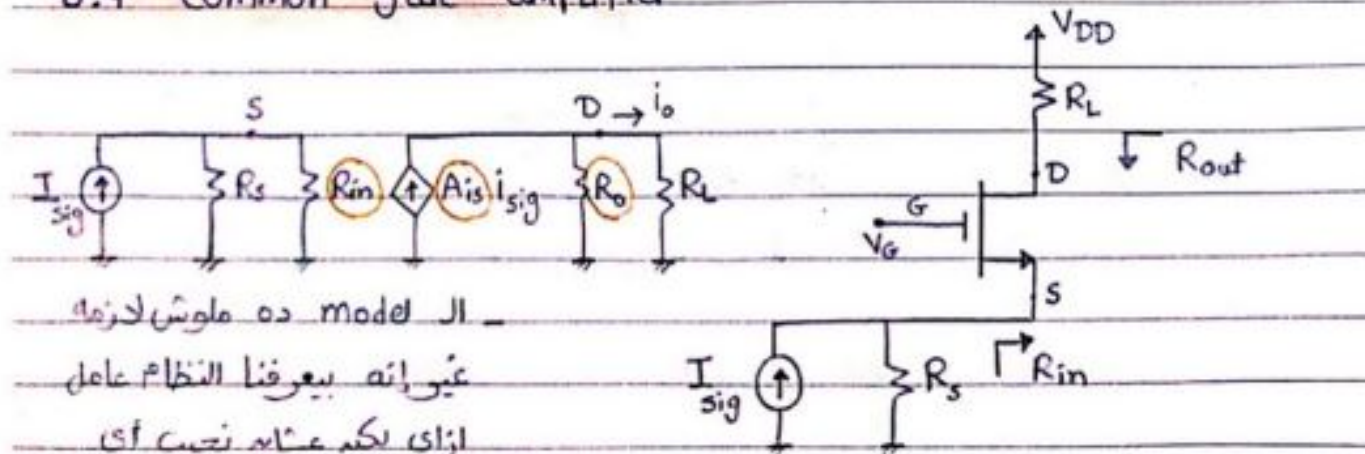

ال model ده ماوش لازمه

غيراته بغيرنا النظام عامل

ازاي بكم عتاده نجيب اى

حاجه بكونه مع ال model ده

احنا عارفينه

Elzahraa

R_{in}, R_{out}, A_v


$$V_x = (i_x + g_m V_{gs}) r_o + i_x R_L \quad \text{--- (1)}$$

$$\therefore V_{gs} = V_D - V_S = -V_S \quad \therefore V_x = V_S \quad \therefore V_{gs} = -V_x$$

$$\therefore V_x = i_x r_o - g_m V_x r_o + i_x R_L$$

$$\therefore V_x [1 + g_m r_o] = i_x [r_o + R_L]$$
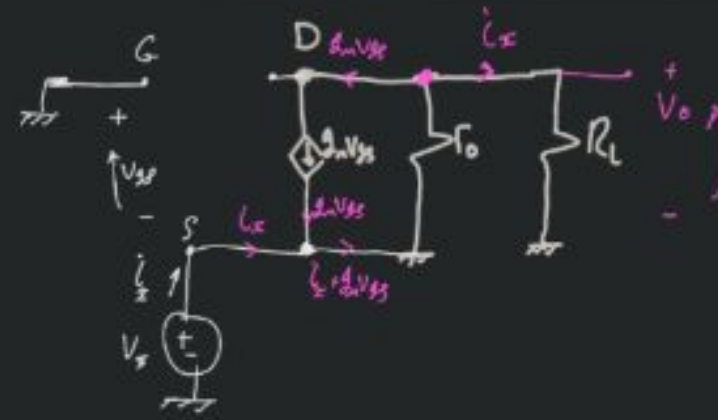
$$\therefore R_{in} = \frac{V_x}{i_x} = \frac{r_o + R_L}{1 + g_m r_o} \quad R_{in} \approx \frac{1}{g_m}$$



$$A_{is} = \frac{i_o}{i_i} \bigg|_{R_L=0} \quad , \quad V_{gs} = V_D - V_S = -V_S$$

$$\textcircled{1} \quad i_i - \frac{V_S}{R_S} = i_o$$

$$\therefore i_i + \frac{V_{gs}}{R_S} = i_o \quad \text{--- (1)}$$


$$\textcircled{2} \quad i_o + g_m V_{gs} + \frac{V_{gs}}{r_o} = 0 \quad \text{--- (2)}$$

From (2)

$$V_{gs} = (i_o - i_i) R_S$$

$$\therefore i_o + g_m (i_o - i_i) R_S + \frac{(i_o - i_i) R_S}{r_o} = 0$$
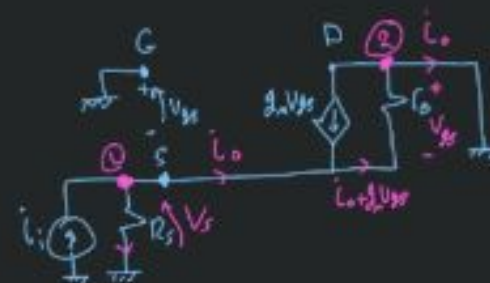
$$\therefore i_o \left[1 + g_m R_S + \frac{R_S}{r_o} \right] = i_i \left[+g_m R_S + \frac{R_S}{r_o} \right] \quad \therefore A_{is} = \frac{i_o}{i_i} = \frac{g_m R_S + R_S/r_o}{1 + g_m R_S + R_S/r_o} \quad \text{--- (3)}$$




R_o

$$V_x = (i_x + g_m V_{gs}) r_o + i_x R_S = 0 \quad \text{--- (1)}$$

$$\therefore i_x = \frac{V_x}{R_S} = -\frac{V_{gs}}{R_S} \quad \therefore V_{gs} = -i_x R_S$$

$$\therefore V_x = i_x r_o + i_x g_m R_S + i_x R_S = 0$$
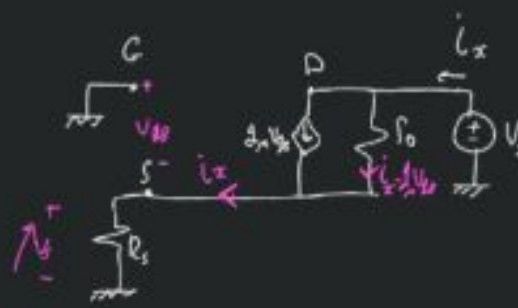
$$\therefore V_x = i_x [r_o + g_m R_S + R_S] \quad \therefore R_o = \frac{V_x}{i_x} = r_o + g_m R_S + R_S \quad \text{--- (2)} \quad \therefore R_o \approx g_m r_o R_S$$



Cascode amplifier:

→ is a CG amp. but its $R_{in} \neq \infty$, so we use it with CS amp who has $R_{in} = \infty$

So there is no current drop at i/p. the cascode gain higher.

• Q_1 : CS, Q_2 : CG

• $R_{in} = R_{in}(Q_1) = \infty$

$$A_{is}(CG) = \frac{g_m R_s + R_s/r_o}{1 + g_m R_s + R_s/r_o} \approx \frac{g_m R_s}{g_m R_s} = 1 \quad "r_o \gg"$$

$$R_o(CG) = g_{m2} r_{o2} R_s = g_{m2} r_{o2} r_{o1}$$

$$\therefore A_{v_o} = -g_{m1} R_o(CG)$$

$$\therefore A_{v_o} = -g_{m1} (g_{m2} r_{o2} r_{o1})$$




$$\therefore A_{v_o} = - (g_{m1} r_{o1}) (g_{m2} r_{o2})$$


$$\therefore A_{v_o} = - A_{v_{o1}} \cdot A_{v_{o2}}$$

if $g_{m1} = g_{m2}$, $r_{o1} = r_{o2} \rightarrow A_v = -A_{v_o}^2 \quad \uparrow\uparrow \quad 2\text{-times intrinsic gain } \uparrow\uparrow$

→ the gain $\uparrow\uparrow$ in this case because we used ideal c.s $r_o \approx \infty$, it's practical equivalent is c.s PMOS.

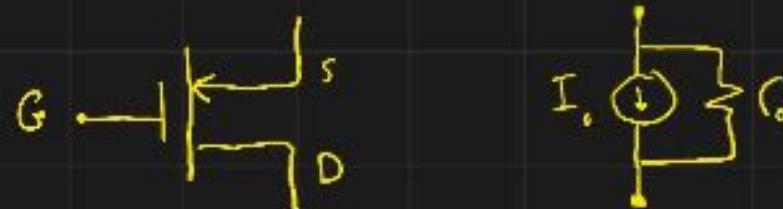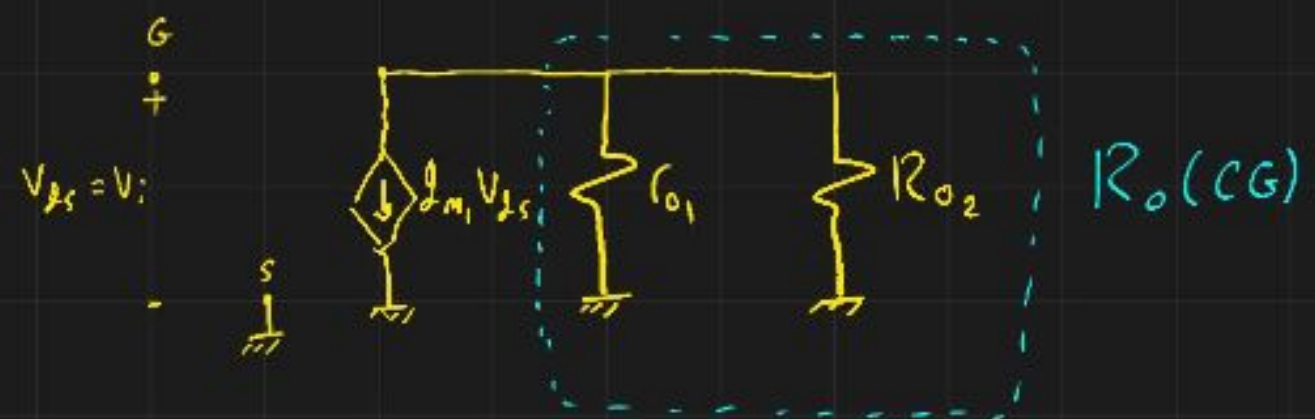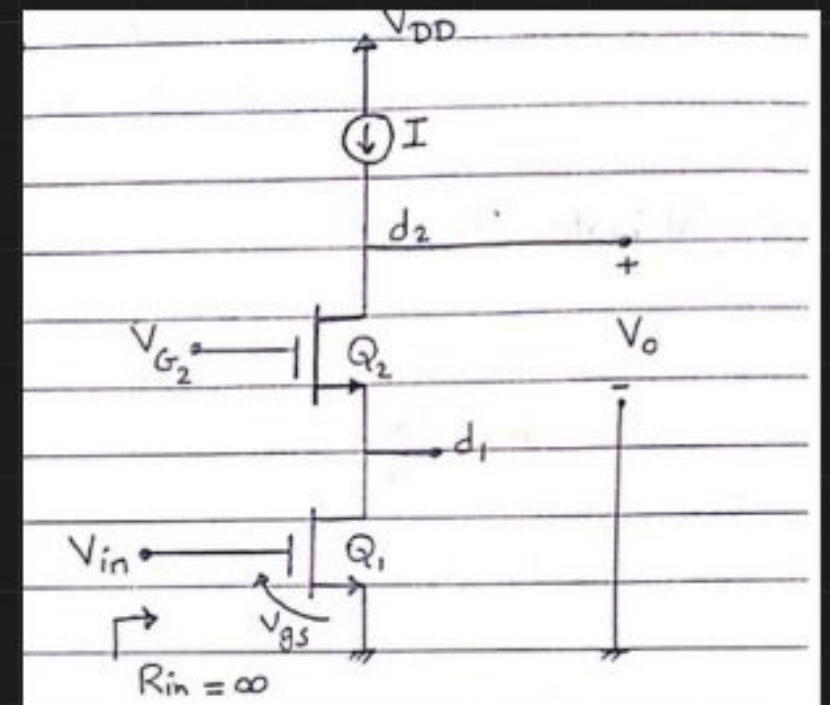
→ also the MOS will drive constant current.



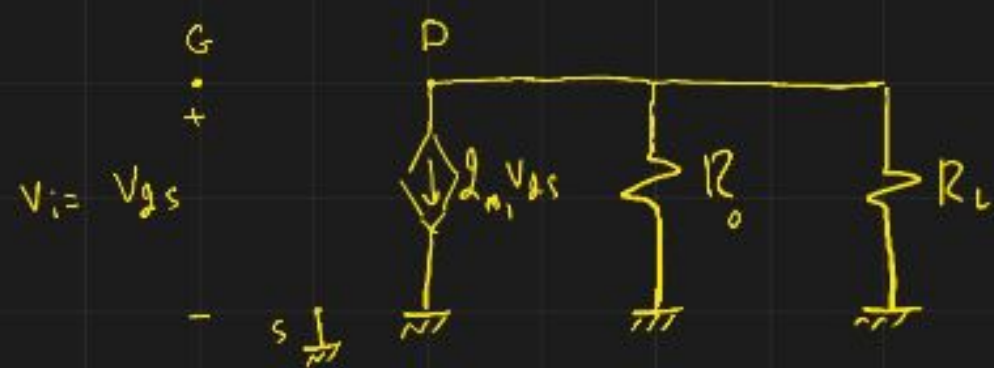

* CasCode Loaded with PMOS

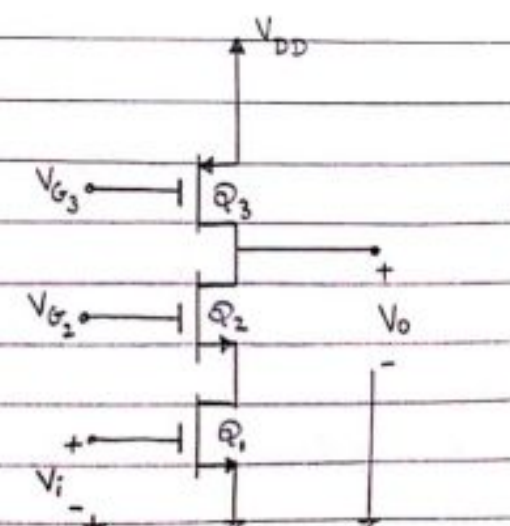Q_1 : Common Source
 Q_2 : Common Gate } CasCode
 Q_3 : Load



$$\rightarrow R_o = R_o(Q_2) = g_{m2} r_{o2} R_s = g_{m2} r_{o2} r_{o1}$$

$\rightarrow R_L$: is the resistance at the drain of Q_2 \rightarrow which is $r_{o3} \rightarrow \therefore R_L = r_{o3}$


$$\therefore A_v = -g_{m1} (R_o \parallel R_L)$$

$$\therefore A_v = -g_{m1} [(g_{m2} r_{o2} r_{o1} \parallel r_{o3})]$$

if $r_{o1} = r_{o2} = r_{o3} = r_o \rightarrow \therefore g_{m2} r_{o2} r_{o1} \gg r_{o3} \rightarrow \therefore A_v = -g_{m1} r_o \downarrow \downarrow$

* CasCode with 2 PMOS as load:

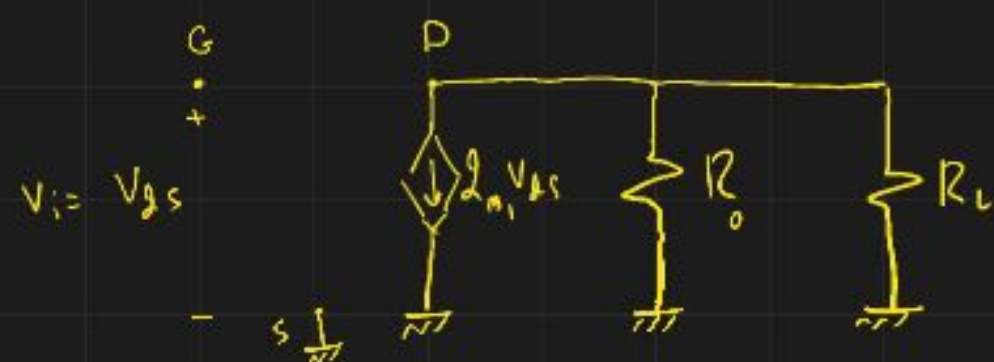\rightarrow the gain has decreased $\downarrow \downarrow$, to increase it we'll use 2 PMOS as Load.



$\rightarrow Q_1, Q_2$ are C.S followed by C.G (NMOS)

$$\hookrightarrow R_o = g_{m2} r_{o2} R_s = g_{m2} r_{o2} r_{o1} \rightarrow R_o$$

$\rightarrow Q_3, Q_4$ are C.S followed by C.G (PMOS)


$$\hookrightarrow R_{op} = g_{m3} r_{o3} R_s = g_{m3} r_{o3} r_{o4} \rightarrow R_L$$

$$\therefore A_v = -g_{m1} (R_o \parallel R_{op})$$

$$\therefore A_v = -g_{m1} (g_{m2} r_{o2} r_{o1} \parallel g_{m3} r_{o3} r_{o4})$$

\rightarrow if $g_{m1} = g_{m2} = g_{m3} = g_{m4} = g_m$ and $r_{o1} = r_{o2} = r_{o3} = r_{o4} = r_o$
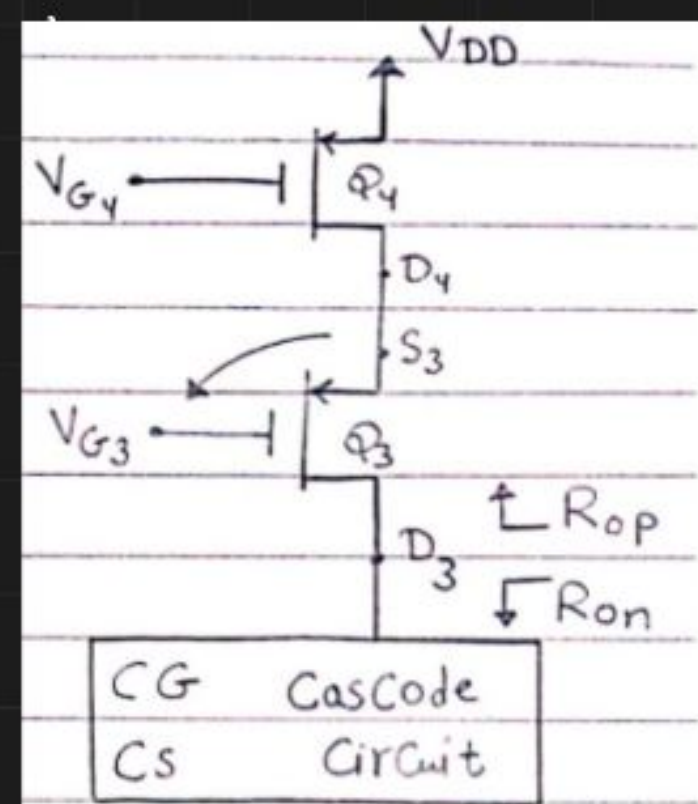
$$\hookrightarrow A_v = \frac{1}{2} g_m^2 r_o^2 = -\frac{1}{2} A_{v0} \uparrow \uparrow$$



Ex (8.4) Very important Page (573) على اليمين المرفقات

Design a Cascode Current Source to Provide a Current of $100 \mu A$ and an o/p resistance of $500 k\Omega$, assume the availability of $0.18 \mu m$ CMOS technology for which $V_{DD} = 1.8 V$, $V_{tp} = -0.5 V$, $\mu_p C_{ox} = 90 \mu A/V^2$ and $V_A = -5 V/\mu m$. use $|V_{ov}| = 0.3 V$ and determine L and W/L for each transistor, and the values of the bias voltage V_{G3} , V_{G4} .

$I_D = 100 \mu A$ $\mu_p C_{ox} = 90 \mu A/V^2$
 $R_{out} = 500 k\Omega$ $V_A = -5 V/\mu m \rightarrow V_A = V_A L$
 $V_{DD} = 1.8 V$ $|V_{ov}| = 0.3 V$
 $V_{tp} = -0.5 V$ $Q_3 \& Q_4$ are matched
 find: L , $\frac{W}{L}$, V_{G3} , V_{G4}

$$R_{op} = g_{m3} r_{o3} r_{o4} \quad \because Q_3, Q_4 \text{ matched}$$

$$R_{op} = g_{m3} r_o^2 \rightarrow (1) \quad r_{o3} = r_{o4} = r_o$$

$$g_{m3} = \frac{2 I_D}{|V_{ov}|} \rightarrow (2)$$

$$r_o = \frac{|V_A|}{I_D} \rightarrow (3)$$

from (1), (2), (3)

$$R_{op} = \frac{2 I_D}{|V_{ov}|} \cdot \left(\frac{|V_A|}{I_D} \right)^2 = \frac{2 |V_A|^2 L^2}{|V_{ov}| I_D}$$

$$500 \times 10^3 = \frac{2 (-5)^2 \times 10^{12} L^2}{10.3 \times 100 \times 10^{-6}} \quad L^2 = 3 \times 10^{-13}$$

$$L = 5.478 \times 10^{-7} m$$

$$L = 0.56 \mu m$$

$$V_{SG4} = |V_{tp}| + |V_{ov}|$$

$$= 0.5 + 0.3 = 0.8 V$$

$$V_{SG4} = V_{S4} - V_{G4} \quad V_{S4} = V_{DD} = 1.8 V$$

$$0.8 = 1.8 - V_{G4}$$

$$V_{G4} = 1 V$$

* for saturation :-

$$V_{SD4} \geq |V_{ov}| = 0.3 \quad V_{S4} - V_{D4} \geq 0.3$$

$$V_{SD3} \geq |V_{ov}| = 0.3 \quad 1.8$$

$$V_{S3} - V_{D3} \geq 0.3 \quad V_{D4} \leq 1.5 V$$

$$V_{D4} = 1.5 \quad V_{D4} \leq 1.2 V$$

$$V_{SG4} = V_{SG3} = V_{S3} - V_{G3}$$

$$0.8 = 1.5 - V_{G3}$$

$$V_{G3} = 0.7 V$$

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} |V_{ov}|^2 (1 + \lambda V_{SD})$$

$$\lambda = \frac{1}{|V_A|}$$

$$100 \mu A = \frac{1}{2} 90 \mu \frac{W}{L} (0.3)^2 \left(1 + \frac{0.3}{|V_A|} \right)$$

$$|V_A| = |V_A| L = 5 (0.55) = 2.75 V$$

$$V_A = 2.75 V$$

$$\frac{W}{L} = 22.3$$