

* Mos Differential Pair

• Q_1, Q_2 are matched


• $V_{G1} = V_{CM} + \frac{V_{id}}{2} \rightarrow \textcircled{1}$

• $V_{G2} = V_{CM} - \frac{V_{id}}{2} \rightarrow \textcircled{2}$

• V_{CM} : Common mode input voltage

• V_{id} : differential input voltage

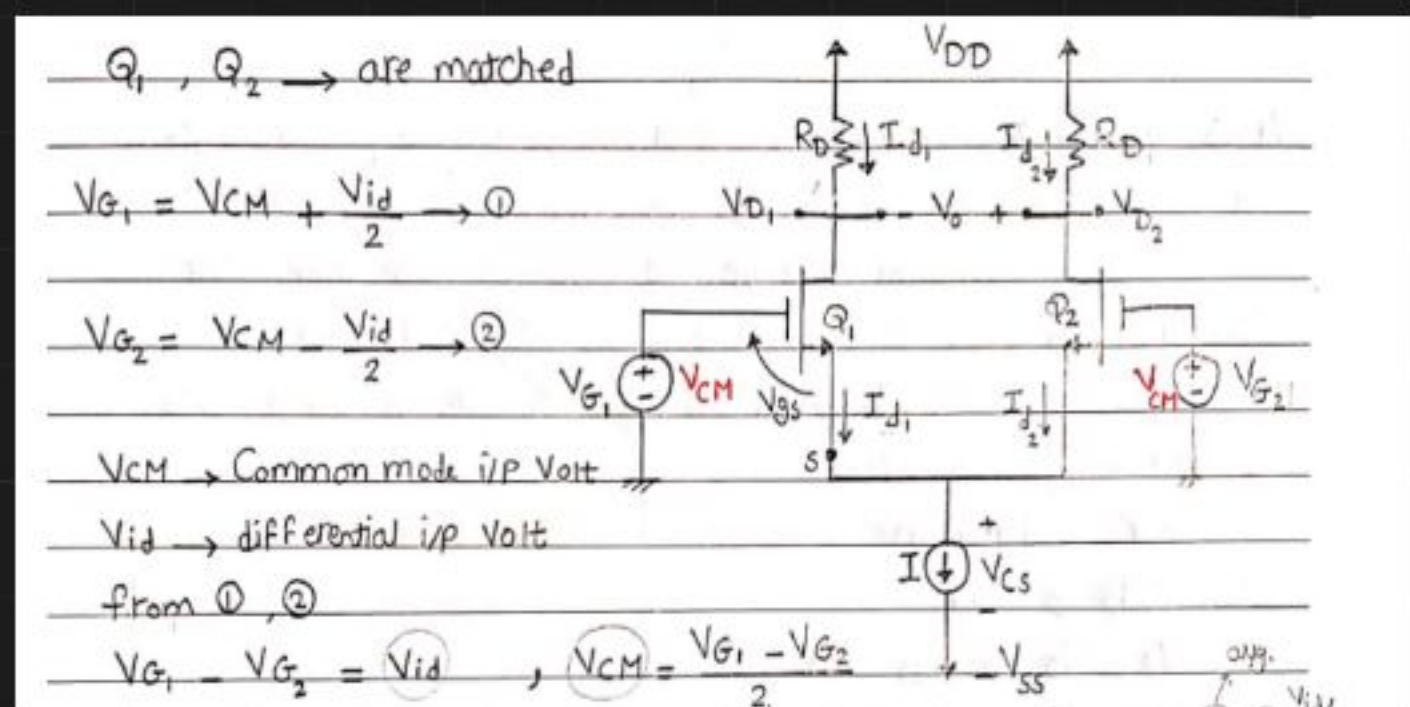$\textcircled{1} - \textcircled{2} \Rightarrow V_{G2} - V_{G1} = V_{id} \quad , \quad V_{CM} = \frac{V_{G2} - V_{G1}}{2}$



① Common mode operation:

$\rightarrow V_{G1} = V_{G2} = V_{CM}$

$\rightarrow I_{D1} + I_{D2} = I \quad , \quad I_{D1} = I_{D2} = \frac{I}{2}$

$\rightarrow V_{GS1} = V_{GS2}$ "Matched" , $V_S = V_{CM} - V_{GS}$

$\rightarrow V_{D1} = V_{D2} = V_{DD} - I_D R_D \quad \rightarrow V_O = V_{D1} - V_{D2} = 0$

$\rightarrow I_{D1} = \frac{1}{2} K_n (V_{GS} - V_t)^2$

$\rightarrow I_{D2} = \frac{1}{2} K_n (V_{GS} - V_t)^2$

• in order for the Common mode to work, V_{CM} must lay in some range

$\therefore V_{DS} \geq V_{OV}$ "Saturation"

$\therefore V_D - V_S \geq V_{GS} - V_t$

$\therefore V_D - V_S \geq V_G - V_t$

$\therefore V_D \geq V_G - V_t$

$\therefore V_D \geq V_{CM} - V_t$

$\therefore V_{CM} \leq V_D + V_t$

$\therefore V_G = V_{CM}$

$\therefore V_{CM_{max}} = V_D + V_t$

$\therefore V_D = V_{DD} - \frac{I}{2} R_D$

$V_{CM_{max}} = V_{DD} - \frac{I}{2} R_D + V_t$

• in order for the CS to work the voltage drop across > 0

$\rightarrow V_S - V_{CS} + V_{SS} > 0$

$\therefore V_{CS} < V_S + V_{SS}$


$\therefore V_S = V_{CM} - V_{GS}$

$\therefore V_{CS} < V_{CM} - V_{GS} + V_{SS}$

$\therefore V_{CM} > V_{CS} + V_{GS} - V_{SS}$

$\therefore V_{CM} > V_{CS} - V_{SS} + V_{OV} + V_t$

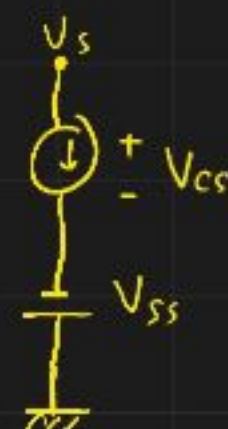$V_{CM_{min}} = V_{CS} + V_{OV} + V_t - V_{SS}$




$\therefore V_{CM_{min}} < V_{CM} < V_{CM_{max}}$

Ex (9.1) Page (609) Very important

for The Mos diff. Pair with V_{CM} applied $V_{DD} = V_{SS} = 1.5V$
 $K_n(W) = 4 mA/V^2$, $V_t = 0.5V$, $I = 0.4mA$, $R_D = 2.5K\Omega$
 neglect Channel length modulation ($\lambda = 0$). assume The C.S
 (I) requires min Voltage of $0.4V$ ($V_{CS} = 0.4V$)

ترتيب الأسئلة في الكتاب مختلف عما في موقعنا المقصود نجيب ال
 range يتبع ال V_{CM} عما نفرض هنا ولا لا والدكتور قال يجب
 كده في الامتحان نجيب ال range وبعد كده نبدأ نحل

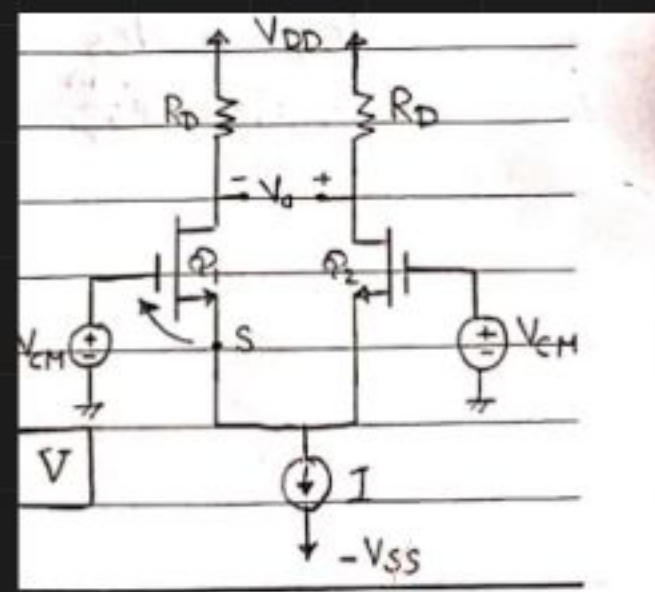① find V_{ov} , V_{GS} for each transistor



$$\therefore I_{D1} = I_{D2} = \frac{I}{2} = \frac{0.4}{2} = 0.2mA$$

$$\therefore I_D = \frac{1}{2} K_n (V_{ov})^2$$

$$\therefore 0.2mA = \frac{1}{2} (4mA/V^2) (V_{ov})^2 \rightarrow V_{ov} = 0.32V \rightarrow V_{GS} = V_{ov} + V_t = 0.32 + 0.5 \rightarrow V_{GS} = 0.82V$$

$$Q_1, Q_2 \text{ matched} \rightarrow V_{GS1} = V_{GS2}, V_{ov1} = V_{ov2}$$


② for $V_{CM} = 0$, find V_S , I_{D1} , I_{D2} , V_{D1} , V_{D2} , V_O

$$\rightarrow \therefore V_S = V_{CM} - V_{GS} \rightarrow \therefore V_S = 0 - 0.82V \rightarrow V_S = -0.82V \text{ use same } V_{GS}?, \text{ yes because } I/2 \text{ is constant}$$

$$\rightarrow I_{D1} = I_{D2} = \frac{I}{2} = 0.2mA$$

$$\rightarrow V_{D1} = V_{D2} = V_{DD} - \frac{1}{2} I R_D \rightarrow \therefore V_D = 1.5 - 0.2(2.5) \rightarrow V_{D1} = V_{D2} = 1V$$
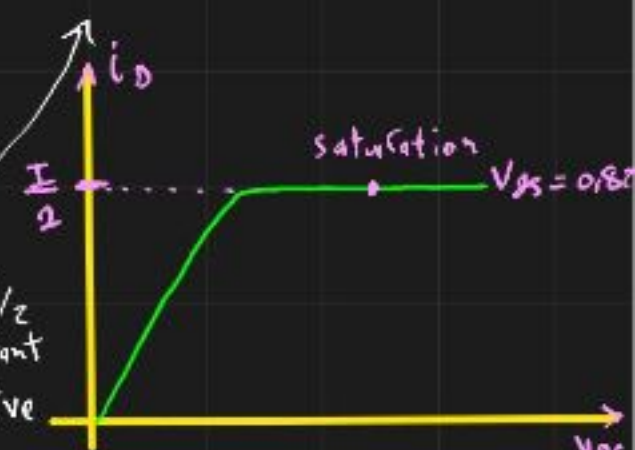
$$\rightarrow V_O = V_{D2} - V_{D1} = 0$$



to Make sure in Saturation

$$\rightarrow V_{DS} = V_D - V_S = 1 - (-0.82)$$

$$\therefore V_{DS} = 1.82 > V_{ov} \checkmark$$

to Make sure C.S works

$$V_{CS} = V_S + V_{SS} = -0.82 + 1.5$$

$$\therefore V_{CS} = 0.68V > V_{CM} = 0.4V_{min} \checkmark$$

③ Repeat ② @ $V_{CM} = 1V$

$$\therefore V_S = V_{CM} - V_{GS} = 1 - 0.82 \rightarrow \therefore V_S = 0.18V$$

$$\therefore V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D = 1.5 - 0.2(2.5) \rightarrow \therefore V_{D1} = V_{D2} = 1V$$

→ check Saturation

$$\rightarrow V_{DS} = V_D - V_S = 1 - 0.18 \rightarrow \therefore V_{DS} = 0.82V > V_{ov} \checkmark$$

→ no need to check V_{CS} here, because we increased $V_{CM} \uparrow \rightarrow V_S \uparrow \rightarrow V_{CS} \uparrow$

and it was already working.

④ a) $V_{CM} = -0.2 \text{ V}$

→ We decreased $V_{cm} \rightarrow V_s \downarrow \rightarrow V_{cs} \downarrow$ might not work needs to check
 $\rightarrow V_{ds} \uparrow$ no need to check saturation

$V_s = V_{cm} - V_{cs} = -0.2 - 0.82 \rightarrow \therefore V_s = -1.02 \text{ V}$

$V_{cs} = V_s + V_{ss} = -1.02 + 1.5 \rightarrow \therefore V_{cs} = 0.48 \text{ V} > V_{cs_{min}} \checkmark$

$V_{D1} = V_{D2} = 1 \text{ V}$

$I_{D1} = I_{D2} = 0.2 \text{ mA}$

⑤ highest permitted value of V_{CM} ($V_{CM_{max}}$)

$V_{ds} \geq V_{ov}$

$\therefore V_{ds} \geq V_{gs} - V_t$

$\therefore V_D - V_s \geq V_G - V_s - V_t$

$\therefore V_D \geq V_G - V_t$

$\therefore V_D \geq V_{cm} - V_t$

$\therefore V_{cm} \leq V_D + V_t$

$\therefore V_{CM_{max}} = V_D + V_t$
 $= 1 + 0.5$

$\therefore V_{CM_{max}} = 1.5$

⑥ Lowest Value of V_{CM} ($V_{CM_{min}}$)

$V_s - V_{cs} + V_{ss} > 0$

$\therefore V_{cs} < V_s + V_{ss}$

$\therefore V_{cs} < V_{cm} - V_{gs} + V_{ss}$

$\therefore V_{cm} > V_{cs} + V_{gs} - V_{ss}$

$\therefore V_{CM_{min}} = V_{cs_{min}} + V_{gs} - V_{ss}$

$= 0.4 + 0.82 - 1.5$

$\therefore V_{CM_{min}} = -0.28 \text{ V}$

$\therefore -0.28 < V_{cm} < 1.5$



