

Prob. (9.20)




Find the diff. half circuit, derive an expression for A_d

$$A_d = \frac{V_{od}}{V_{id}} = f(g_m, R_D, R_s) \text{, neglect early effect.}$$

no f_o

1 → What is the gain $R_s = 0 \rightarrow A_{d\max}$

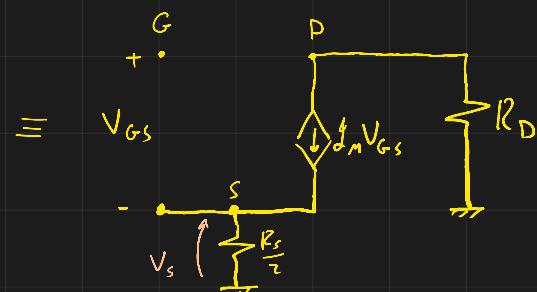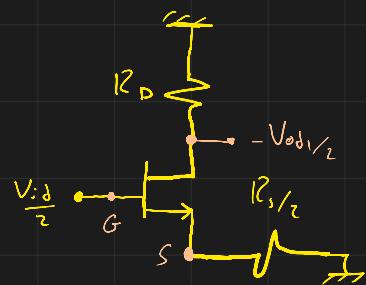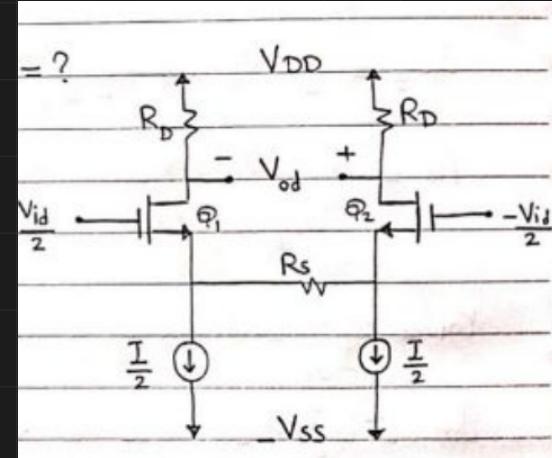2 → " " " Value of R_s $f(\frac{1}{g_m})$ that reduce gain to half value



$$\textcircled{1} \quad A_d = \frac{V_{od1}}{V_{id1}} = \frac{V_{od1}/2}{V_{id1}/2} = \frac{V_{od1}}{V_{id}} = \frac{V_D}{V_G} = \frac{V_D}{V_{id}/2}$$

$$\rightarrow V_D = -g_m V_{GS} R_D \rightarrow \textcircled{1}$$

$$\rightarrow V_{GS} = V_G - V_S = \frac{V_{id}}{2} - g_m V_{GS} \frac{R_s}{2}$$

$$\therefore V_{GS} + g_m V_{GS} \frac{R_s}{2} = \frac{V_{id}}{2}$$

$$\therefore V_{GS} \left(1 + g_m \frac{R_s}{2} \right) = \frac{V_{id}}{2}$$

$$\therefore V_{GS} = \frac{\frac{V_{id}}{2}}{1 + g_m R_s / 2}$$

$$\therefore \textcircled{1} \rightarrow V_D = -g_m \left(\frac{\frac{V_{id}}{2}}{1 + g_m R_s / 2} \right) R_D$$

$$\therefore A_d = \frac{V_D}{V_{id}/2}$$

$$\therefore A_d = -g_m \frac{1}{1 + g_m R_s / 2} R_D$$

$$\therefore A_{d\max} (R_s = 0) = -g_m R_D$$

$$\textcircled{2} \quad R_s = ? \quad \textcircled{3} \quad A_d = \frac{1}{2} A_{d\max}$$

$$\rightarrow \therefore \cancel{g_m} \frac{1}{1 + g_m R_s / 2} \cancel{R_D} = \frac{1}{2} (-g_m \cancel{R_D})$$

$$\therefore 1 + g_m R_s / 2 = 2 \quad \leadsto \therefore R_s = \frac{2}{g_m}$$

* Large Signal Operation:


$$\therefore I_{D_1} = \frac{1}{2} K_n \left(\frac{\omega}{L} \right) (V_{GS_1} - V_t)^2 \rightarrow (1)$$

$$\therefore I_{D_2} = \frac{1}{2} K_n \left(\frac{\omega}{L} \right) (V_{GS_2} - V_t)^2 \rightarrow (2)$$

Root of (1), (2):

$$\therefore \sqrt{I_{D_1}} = \sqrt{\frac{1}{2} K_n \left(\frac{\omega}{L} \right)} (V_{GS_1} - V_t) \rightarrow \therefore \sqrt{I_{D_1}} = \sqrt{\frac{1}{2} V_{ov}} (V_{GS_1} - V_t) \rightarrow (3)$$
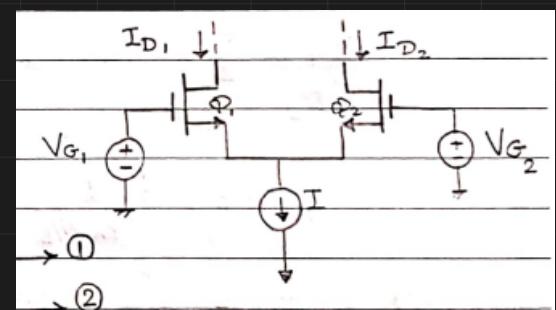
$$\therefore \sqrt{I_{D_2}} = \sqrt{\frac{1}{2} K_n \left(\frac{\omega}{L} \right)} (V_{GS_2} - V_t) \rightarrow \therefore \sqrt{I_{D_2}} = \sqrt{\frac{1}{2} V_{ov}} (V_{GS_2} - V_t) \rightarrow (4)$$



$$(3) - (4) \rightarrow \therefore \sqrt{I_{D_1}} - \sqrt{I_{D_2}} = \sqrt{\frac{1}{2} V_{ov}} (V_{GS_1} - V_{GS_2})$$

$$\therefore \sqrt{I_{D_1}} - \sqrt{I_{D_2}} = \sqrt{\frac{1}{2} V_{ov}} (V_{id}) \rightarrow (5)$$

$$(5)^2 \rightarrow I_{D_1} + I_{D_2} - 2\sqrt{I_{D_1} I_{D_2}} = \frac{1}{2} V_{ov} (V_{id})^2 \quad \therefore I_{D_1} + I_{D_2} = I$$

$$\therefore I - 2\sqrt{I_{D_1} I_{D_2}} = \frac{1}{2} V_{ov} (V_{id})^2 \rightarrow (6)$$

∴ to get I_{D_1} ,

$$(6) \rightarrow I - 2\sqrt{I_{D_1} I_{D_2}} = \frac{1}{2} V_{ov} (V_{id})^2$$

$$\therefore I_{D_1} = \frac{I}{2} + \frac{I}{V_{ov}} \left(\frac{V_{id}}{2} \right) \sqrt{1 - \left(\frac{V_{id}}{2V_{ov}} \right)^2}$$

$$\therefore I_{D_2} = \frac{I}{2} - \frac{I}{V_{ov}} \left(\frac{V_{id}}{2} \right) \sqrt{1 - \left(\frac{V_{id}}{2V_{ov}} \right)^2}$$

→ note:


$$\hookrightarrow V_{id} > 0 \rightarrow V_{GS_1} > V_{GS_2} \rightarrow I_{D_1} = \frac{I}{2} + \dots$$

$$I_{D_2} = \frac{I}{2} - \dots$$

$$\hookrightarrow V_{id} < 0 \rightarrow V_{GS_2} > V_{GS_1} \rightarrow I_{D_1} = \frac{I}{2} - \dots$$

$$I_{D_2} = \frac{I}{2} + \dots$$
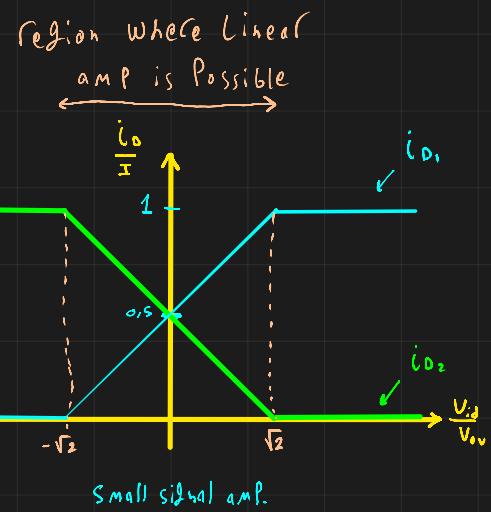
$$\hookrightarrow V_{id} = 0 \rightarrow \text{Common Mode} \rightarrow I_{D_1} = I_{D_2} = \frac{I}{2}$$



$$\begin{aligned} I_{D_1} (V_{id} = \sqrt{2} V_{ov}) &= \frac{I}{2} + \frac{I}{V_{ov}} \left(\frac{\sqrt{2} V_{ov}}{2} \right) \sqrt{1 - \left(\frac{\sqrt{2} V_{ov}}{2V_{ov}} \right)^2} \\ &= \frac{I}{2} + \frac{I}{2} \\ &= I \end{aligned}$$

* Small Signal operation:

$$\rightarrow V_{id} < \sqrt{2} V_{ov}$$

$$\rightarrow i_{D_1} = \frac{I}{2} + \frac{I}{V_{ov}} \left(\frac{V_{id}}{2} \right) \sqrt{1 - \left(\frac{V_{id}}{2V_{ov}} \right)^2}$$

$$= \frac{I}{2} + \frac{I}{V_{ov}} \left(\frac{V_{id}}{2} \right) \left(1 - \frac{1}{2} \left(\frac{V_{id}}{2V_{ov}} \right)^2 \right)$$

$$= \frac{I}{2} + \left(\frac{I}{2} \right) \left[\frac{V_{id}}{V_{ov}} - \frac{1}{4} \left(\frac{V_{id}}{V_{ov}} \right)^2 \right] \xrightarrow{D}$$

$$= \frac{I}{2} + \frac{I}{V_{ov}} \left(\frac{V_{id}}{2} \right)$$

$$\therefore i_{D_1} = \frac{I}{2} + g_m \left(\frac{V_{id}}{2} \right)$$


$$\therefore i_{D_2} = \frac{I}{2} - g_m \left(\frac{V_{id}}{2} \right)$$

$$\therefore i_d = g_m \left(\frac{V_{id}}{2} \right)$$

→ Notes:

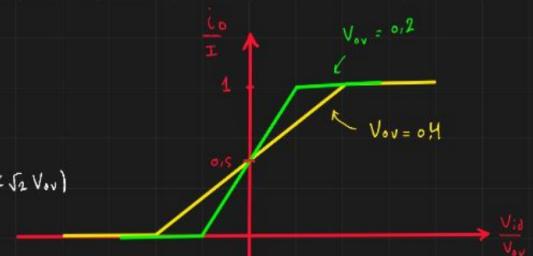1) increasing V_{ov} extends the Linear Range ($-V_{ov} < V_{id} < V_{ov}$)

(Tradeoff: decrease in Gain ($g_m \downarrow \rightarrow g_m = \frac{2I}{V_{ov}}$))



2) decrease V_{ov} gain ↑ but linear region ↓

3) we can increase I (bias current) to increase gain

(Tradeoff: higher power dissipation.)

$$0.18 \mu\text{m CMOS} \quad M_n C_{ox} = 4 \mu p C_{ox} = 400 \mu\text{A/V}^2$$


$$|V_{t1}| = 0.5 \text{ V}$$

$$I = 200 \text{ nA}$$

$$|V_{ov1}| = 0.2 \text{ V}$$

find : * $\frac{W}{L}$ for $\text{Q}_1, \text{Q}_2, \text{Q}_3, \text{Q}_4$

* the differential voltage gain A_d

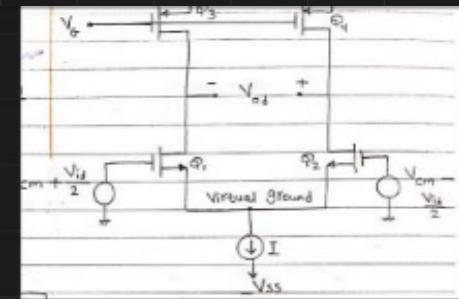

$$\cdot I_{D1} = I_{D2} = \frac{I}{2} = \frac{200}{2} = 100 \text{ nA}$$

$$\cdot I_D = \frac{1}{2} K_n (\frac{W}{L})_1 (V_{ov1})^2$$

$$\therefore 100 \mu = \frac{1}{2} (400 \mu) (\frac{W}{L})_1 (0.2)^2$$

$$\therefore (\frac{W}{L})_1 = (\frac{W}{L})_2 = 12.5$$

$$I_D = \frac{1}{2} K_n (\frac{W}{L})_3 (V_{ov3})^2$$

$$100 \mu = \frac{1}{2} (100 \mu) (\frac{W}{L})_3 (0.2)^2$$

$$\therefore (\frac{W}{L})_3 = (\frac{W}{L})_4 = 50$$

$$\cdot A_d = -g_m (\text{f}_o \parallel \text{f}_o)$$

$$\rightarrow f_o = \frac{V_A}{I_D} = \frac{V_A L}{I_D} = \frac{(10)(0.36)}{100 \mu} = 36 \text{ k}\Omega$$

$$\rightarrow f_o = \frac{V_A L}{I_D} = \frac{(10)(0.36)}{100 \mu} = 36 \text{ k}\Omega$$

$$\rightarrow g_m = \frac{2I_D}{V_{ov}} = \frac{I}{V_{ov}} = \frac{200 \mu}{0.2} = 1 \text{ mA/V}$$

$$\therefore A_d = - (1) (\frac{1}{2} + 36) \rightarrow A_d = -18$$

Ex (9.6) CasCode diff. amplifier

$$M_n C_{ox} = 4 \mu p C_{ox} = 400 \mu\text{A/V}^2$$

$$|V_{t1}| = 0.5 \text{ V}$$

$$|V_{A1}| = 10 \text{ V/}\mu\text{m}$$

$$I = 200 \text{ nA} \quad L = 0.36 \mu\text{m}$$

$$|V_{ov1}| = 0.2 \text{ V}$$

find : ① $\frac{W}{L}$ for each of $\text{Q}_1 \rightarrow \text{Q}_8$ ② A_d

$$\cdot I_{D1} = \frac{1}{2} K_n (\frac{W}{L})_1 (V_{ov1})^2$$

$$100 \mu = \frac{1}{2} (400 \mu) (\frac{W}{L})_1 (0.2)^2$$

$$\therefore (\frac{W}{L})_{1,2,3,4} = 12.5$$

$$I_{D5} = \frac{1}{2} K_n (\frac{W}{L})_5 (V_{ov5})^2$$

$$100 \mu = \frac{1}{2} (100 \mu) (\frac{W}{L})_5 (0.2)^2$$

$$\therefore (\frac{W}{L})_{5,6,7,8} = 50$$

$$\cdot A_d = -g_m (\text{R}_{on} \parallel \text{R}_{op})$$

$$\text{R}_{on} = g_m f_o f_o$$

$$\text{R}_{op} = g_m f_o f_o$$

$$\cdot f_o = \frac{V_A}{I_D} = \frac{V_A L}{I_D} = 36 \text{ k}\Omega$$

$$\cdot g_m = \frac{2I_D}{V_{ov}} = \frac{I}{V_{ov}} = 1 \text{ mA/V}$$

$$\therefore \text{R}_{on} = 36^2 \text{ k}\Omega$$

$$\therefore \text{R}_{op} = 36^2 \text{ k}\Omega$$

$$\therefore A_d = g_m \frac{36^2}{2} = 648$$

