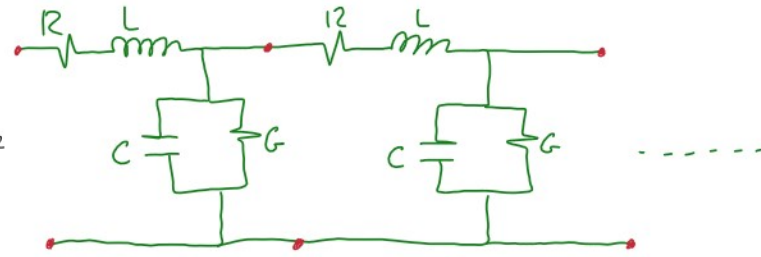


→ at high Freq, the wavelength is small compared with line length.

→ if the TL is uniform, it can be represented as cascaded distributed sections each containing  $R, L, C, G$



→ therefore the series Impedance  $Z$ , and shunt admittance  $Y$ , per meter are given as: (e<sup>jωt</sup> time function)

$$Z = R + j\omega L \quad \Omega/m$$

$$Y = G + j\omega C \quad S/m$$

### Voltage and Current Differential Equations:

Consider a length  $dx$  of the T.L


$i_x, V_x$  in  $\rightarrow i_x + di_x, V_x + dV_x$  out

We expect  $dV_x$  to be negative, because voltage decreases with distance.

$$\rightarrow V_x - (V_x + dV_x) = i_x Z dx \rightarrow \therefore \frac{dV_x}{dx} = -i_x Z \rightarrow (1)$$

$$\rightarrow di_x = -(V_x + dV_x) Y dx$$
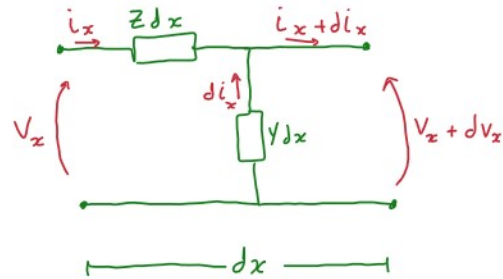
$$= -V_x Y dx - Y dV_x dx \rightarrow \therefore \frac{di_x}{dx} = -V_x Y \rightarrow (2)$$



We have two diff eqs.

$$\rightarrow \frac{\partial}{\partial x} : \frac{\partial V_x}{\partial x^2} = -\frac{\partial i_x}{\partial x} Z$$

$$\frac{\partial^2 V_x}{\partial x^2} = -(-V_x Y) Z$$

$$\therefore \frac{\partial^2 V_x}{\partial x^2} = Z Y V_x$$

$$\begin{cases} \bullet \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)} \\ \bullet \gamma = \sqrt{ZY} \\ \therefore \frac{\partial^2 V}{\partial x^2} = \gamma^2 V_x \rightarrow (3) \end{cases}$$

is called the Propagation Constant and its units is per meter.

- Solving (3)

$$V_x = \underbrace{V_+ e^{-\gamma x}}_{\text{Incident}} + \underbrace{V_- e^{\gamma x}}_{\text{Reflected}} \dots (4)$$

$$I_x = \underbrace{I_+ e^{-\gamma x}}_{\text{Incident}} + \underbrace{I_- e^{\gamma x}}_{\text{Reflected}} \dots (5)$$

### Relations between $V_+, I_+$ and $V_-, I_-$

→ substituting (4), (5) in (1)

$$\therefore -\gamma V_+ e^{-\gamma x} + \gamma V_- e^{\gamma x} = -(I_+ e^{-\gamma x} + I_- e^{\gamma x}) Z$$

$$\therefore -\delta V_+ = -I_+ Z$$

$$\therefore I_+ = \frac{\delta V_+}{Z} = \frac{V_+}{Z/\delta}$$

$$\therefore I_+ = \frac{V_+}{Z_0}$$

$$\therefore \delta V_- = -I_- Z$$

$$\therefore I_- = \frac{-\delta V_-}{Z} = \frac{-V_-}{Z/\delta}$$

$$\therefore I_- = \frac{-V_-}{Z_0}$$

$\frac{Z}{\delta}$  represents an Impedance  $Z_0$  called the characteristic Impedance

$$Z_0 = \frac{Z}{\delta} = \frac{Z}{\sqrt{ZY}} = \sqrt{\frac{Z}{Y}} \Omega$$

$$\therefore V_z = V_+ e^{-\delta x} + V_- e^{\delta x}$$

$$\therefore I_x = \frac{V_+}{Z_0} e^{-\delta x} - \frac{V_-}{Z_0} e^{\delta x}$$

Note:

$$\delta = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

$\rightarrow \alpha$  is called the attenuation Constant and  $\beta$  is the Phase shift.

We have two types of T.Ls

① Ideal "Lossless" T.L


•  $R=0$ ,  $G=0$ , T.L composed of LC circuit

$$\bullet Z = j\omega L, Y = j\omega C$$

$$\bullet \delta = \sqrt{ZY} = \sqrt{j^2 \omega^2 LC} = j\omega \sqrt{LC} = \alpha + j\beta$$

$$\therefore \alpha = 0, \beta = \omega \sqrt{LC} \text{ "Linear with Freq"}$$
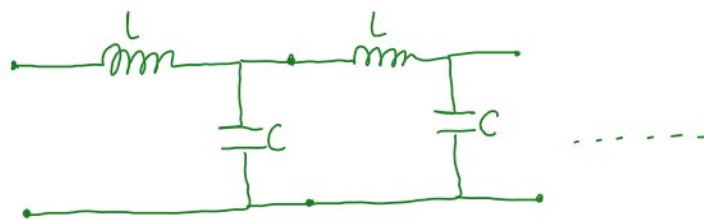
$$\bullet Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}} = R_0 \text{ "Pure Resistive"}$$



② Distortionless T.L

$$\bullet R \neq 0, G \neq 0$$

$$\begin{aligned} \bullet \delta &= \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \sqrt{R(1 + j\omega \frac{L}{R}) \cdot G(1 + j\omega \frac{C}{G})} \end{aligned}$$

$$\bullet \text{Let } \frac{L}{R} = \frac{C}{G} \text{ or } RC = LG$$

$$\therefore \delta = \sqrt{RG(1 + j\omega \frac{L}{R})^2} = \sqrt{RG} (1 + j\omega \frac{L}{R})$$

$$\frac{L^2 G}{R} = \frac{LRC}{R}$$

$$= \sqrt{RG} + j\omega L \sqrt{\frac{G}{R}} = \sqrt{RC} + j\omega \sqrt{LC}$$

$$\therefore \alpha = \sqrt{RC} \text{ Const.} \quad \therefore \beta = \omega \sqrt{LC} \text{ Linear with Freq.}$$

- we have control over  $R, C$  and we design the T.L with  $R, C$  so that  $\alpha \ll$

-  $\beta$  is Linear like in ideal - but we need to make  $\frac{L}{R} = \frac{C}{G}$  to maintain the linearity in  $\beta$ .

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{R(1 + j\omega L/R)}{G(1 + j\omega C/G)}}$$

$$\therefore Z_0 = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}} = R_0 \quad \text{"Pure Resistive"}$$