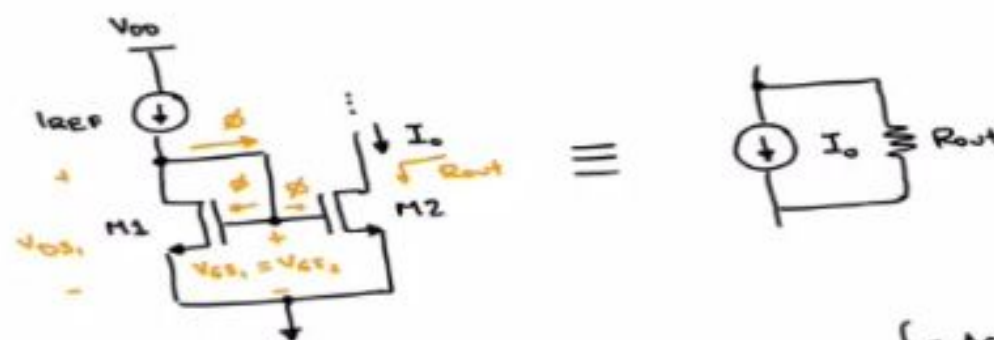


Basic MOSFET Current Mirror



NOTE:
Assume transistors are matched:
 $V_{t1} = V_{t2}$
 $(\mu_n C_{ox})_1 = (\mu_n C_{ox})_2$

Two important parameters to determine performance of current source

- Accuracy (current transfer ratio: I_0 / I_{REF})
- R_{out} (ideally $R_{out} = \infty$, I_0 indep. of loading conditions)

M1 forced into saturation ($V_{DS1} = V_{GS1} > V_{GS1} - V_t$)

$$I_{DS1} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right)_1 (V_{GS1} - V_t)^2 = I_{REF}$$

M2 has same V_{GS} as M1, and therefore, as long as $V_{DS2} \geq V_{GS} - V_t$

$$I_{DS2} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right)_2 (V_{GS1} - V_t)^2 = I_0$$

$$\frac{I_0}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$


Note: More accurate than BJT mirror due to gate current = 0

$$R_{out} = r_{o2} = \frac{1}{\lambda V_{DS2}} = \frac{V_A}{V_{DS2}}$$

Modeling of finite r_o into I_0 eq:

$$\frac{I_0}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1} \cdot \frac{(1 + \lambda V_{DS2})}{(1 + \lambda V_{DS1})}$$

Effects of V_{DS} and r_o in I_0

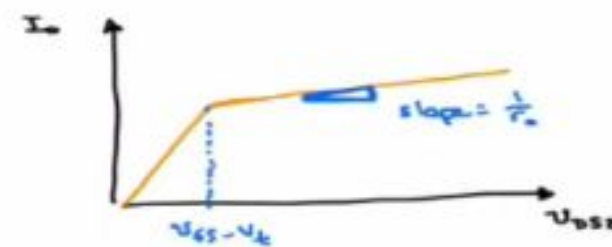


EX (8.1) Page (536)

$$V_{DD} = 3V$$

$$I_{REF} = 100 \mu A$$

$$I_{o, \text{nominal}} = 100 \mu A$$

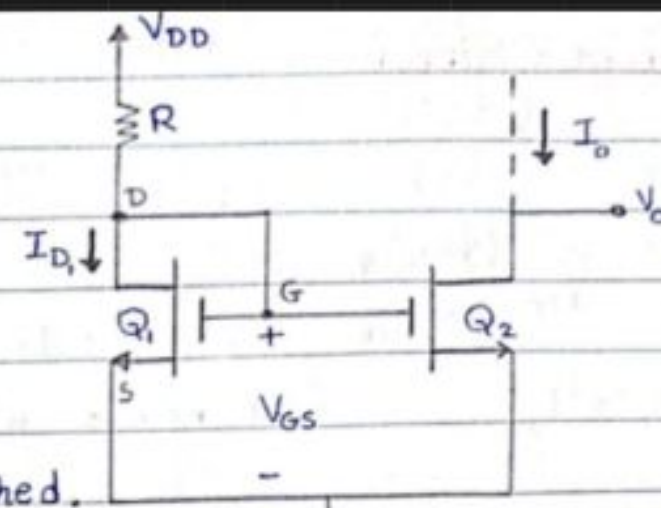

1. find R if Q_1, Q_2 are matched.

$$L = 1 \mu m, W = 10 \mu m, V_t = 0.7V, K_n = 200 \mu A/V^2$$

2. What is The Lowest Value of V_o ? $V_{o, \text{min}}$

3. $V_A = 20V/\mu m$, find The o/p resistance of the Current source.

4. find The Change in o/p Current when $\Delta V_o = 1V$.

$\therefore Q_1, Q_2$ are matched

$$\left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2 \quad I_{o, \text{nominal}} = I_{REF}$$

$$I_{D1} = I_{REF} = \frac{1}{2} K_n \left(\frac{W}{L} \right)_1 V_{ov}^2$$

$$100 \mu A = \frac{1}{2} \times 200 \mu A \left(\frac{10}{1} \right) V_{ov}^2 \quad V_{ov} = 0.316V$$

$$V_{DD} - V_{GS} = I_{REF} R \quad R = \frac{3 - (0.316 + 0.7)}{100 \mu A} = 20K\Omega$$

$$\therefore V_{o, \text{min}} = V_{ov} \quad V_{o, \text{min}} = 0.316V$$

$$\therefore r_{o2} = \frac{V_A}{I_{o, \text{nominal}}} \quad V_A = V_A' L = 20 \times 1 = 20V$$

$$r_{o2} = \frac{20}{100 \mu A} \quad r_{o2} = 200K\Omega$$

$$\therefore \Delta I_o = \frac{\Delta V_o}{r_{o2}} = \frac{1}{200K} \quad \Delta I_o = 5 \mu A$$

Exercise (8.1) Page (536)

In Current source of Ex(8.1), require to reduce ΔI_o when $\Delta V_o = 1V$ to 1% of I_o .

What should the dimensions of Q_1 & Q_2 be changed to?

Q_1 & Q_2 are remain matched

$$I_{o, \text{nominal}} = 100 \mu A$$

$$\Delta V_o = 1V \rightarrow \Delta I_o = 5 \mu A$$

$$\Delta V_o = 1V \rightarrow \Delta I_o = 1 \mu A$$


New

$\Delta I_o \downarrow 5$ times \rightarrow Slope $\downarrow 5$ time

$\therefore \text{Slope} < \text{Slope}_{\text{new}}$

$$r_{o2, \text{new}} > r_{o2}$$

$$r_{o2, \text{new}} = 5 r_{o2}$$

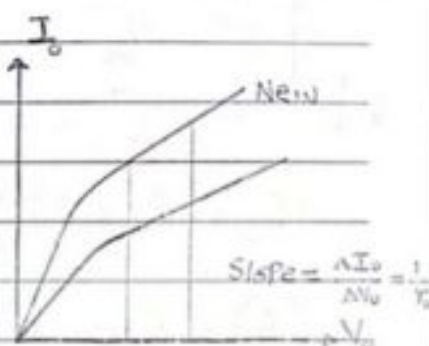

$$R \propto L \quad R = \frac{\rho L}{A} \quad \leftarrow \text{Length زيادة 5 في R}$$

$$L_{\text{new}} = 5L$$

$$\frac{V_A}{I_o} L_{\text{new}} = 5 \frac{V_A}{I_o} L$$

$$I_{o, \text{nominal}} \quad I_{o, \text{nominal}} \quad L_{\text{new}} = 5L$$

$$L_{\text{new}} = 5(1) \mu m = 5 \mu m$$

ثابتة في الحالتين فلا بد W تتغير 5 ما غيرت I_{ref}


$$I_{\text{ref}} = I_{D1} = \frac{1}{2} K_n \left(\frac{W}{L} \right) V_{ov}^2 \quad W \propto L$$

$$W_{\text{new}} = 5W = 5(10) \mu m = 50 \mu m$$

③ Mos. Current Steering Circuits

Q_2 & Q_3 : Current Sink

Q_4 & Q_5 : Current Source

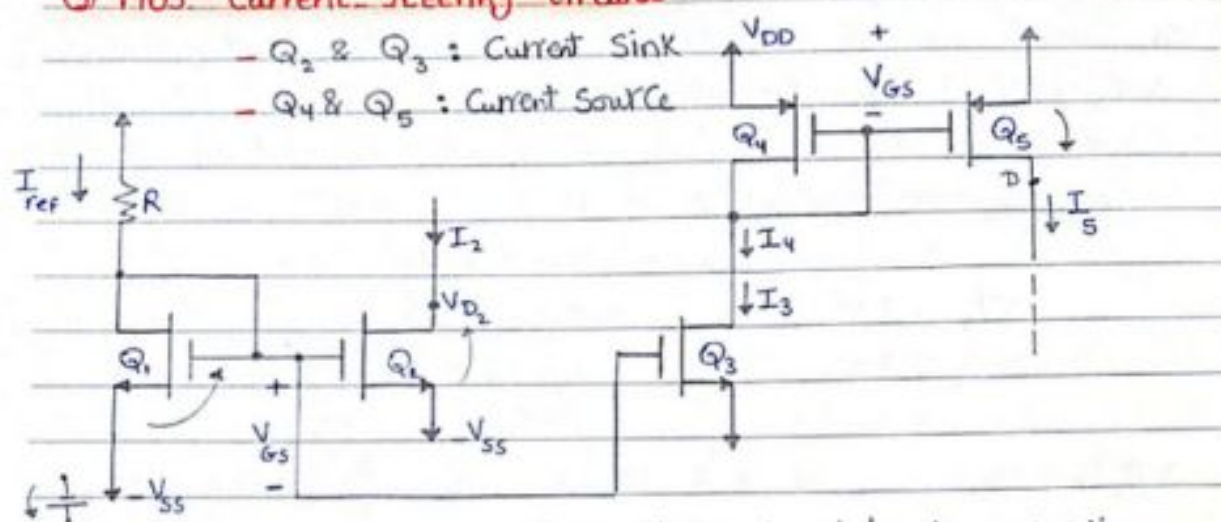

* Each Mos should be in saturation

$$I_2 = I_{\text{ref}} \frac{(W/L)_2}{(W/L)_1}$$

Q_1 & Q_2 & $Q_3 \rightarrow$ NMOS

$$I_3 = I_{\text{ref}} \frac{(W/L)_3}{(W/L)_1}$$

Q_4 & $Q_5 \rightarrow$ PMOS

$V_{D2/3}$

$$V_{D2} \geq V_{ov2} \quad V_{D2} \geq V_{GS2} - V_{tn}$$

$$\therefore V_{D2} = V_{D2} - V_{S2} = V_{D2} - (-V_{SS}) = V_{D2} + V_{SS}$$

$$\therefore V_{D2} \geq -V_{SS} + V_{GS2} - V_{tn}$$

$$V_{D2} \geq -V_{SS} + V_{ov1} \quad \text{for Current Sink}$$

$$I_5 = I_4 \frac{(W/L)_5}{(W/L)_4}$$


$$V_{D5} \leq V_{GS5} - V_{tp} \quad \therefore V_{D5} = V_{D5} - V_{DD}$$

$$V_{D5} - V_{DD} \leq V_{GS5} - V_{tp}$$


$$V_{D5} \leq V_{DD} + V_{GS5} - V_{tp} \quad V_{D5} \leq V_{DD} + V_{ov} \quad (-ve)$$

$$V_{D5} \leq V_{DD} - |V_{ov5}| \quad \text{for Current source}$$

Current Sink

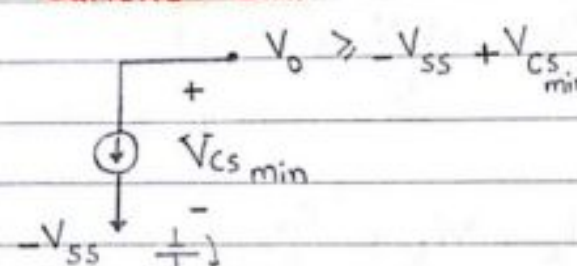

Current Source

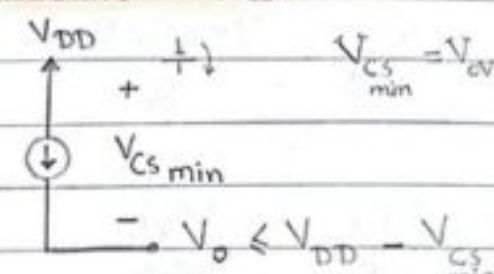

Exercise (8.2) Page (539) Very Important

$$V_{DD} = V_{SS} = 1.5 \text{ V} \quad V_{tn} = 0.6 \text{ V} \quad V_{tp} = -0.6 \text{ V} \quad L = 1 \mu\text{m}$$

$$K_n = 200 \mu\text{A/V}^2 \quad K_p = 80 \mu\text{A/V}^2 \quad \lambda = 0$$

$$I_{ref} = 10 \mu\text{A} \quad I_2 = 60 \mu\text{A} \quad I_3 = 20 \mu\text{A} \quad I_5 = 80 \mu\text{A}$$

→ the Voltage at The drain of Q_2 must be allowed to go down to within 0.2 V of The negative Supply.

→ the Voltage at The drain of Q_5 must be allowed to go up to within 0.2 V of the Positive Supply.

find the widths of all transistors

$$\text{① } -V_e \text{ supply} \rightarrow -V_{SS} \quad Q_2 \rightarrow \text{Sink} \quad V_{ov_1} = 0.2 \text{ V}$$

$$V_{D_2} \gg -V_{SS} + V_{ov_1} \quad V_{D_2} \gg -1.5 + 0.2$$

$$V_{D_2} \gg -1.3 \text{ V}$$

$$\text{② } +V_e \text{ supply} \rightarrow V_{DD} \quad Q_5 \rightarrow \text{Source} \quad |V_{ov_5}| = 0.2 \text{ V}$$

$$V_{D_5} \leq V_{DD} - |V_{ov_5}| \quad V_{D_5} \leq 1.5 - 0.2$$

$$V_{D_5} \leq 1.3 \text{ V}$$

$$I_{ref} = I_{D_1} = \frac{1}{2} K_n \frac{W_1}{L} (V_{ov_1})^2$$

$$10 \mu\text{A} = \frac{1}{2} (200 \mu\text{A}) \frac{W_1}{1} (0.2)^2$$

$$W_1 = 2.5 \mu\text{m}$$

$$I_{D_1} = \frac{V_{DD} - V_G}{R} = \frac{V_{DD} - (V_{GS} - V_{SS})}{R}$$

$$\frac{I_2}{I_{ref}} = \frac{W_2/L}{W_1/L} \quad W_2 = W_1 * \frac{I_2}{I_{ref}} = 2.5 * \frac{60}{10}$$

$$W_2 = 15 \mu\text{m}$$

$$\frac{I_3}{I_{ref}} = \frac{W_3/L}{W_1/L} \quad W_3 = W_1 * \frac{I_3}{I_{ref}} = 2.5 * \frac{20}{10}$$

$$W_3 = 5 \mu\text{m}$$

* from the diff. in The Current

$$10 \mu\text{m} \rightarrow 60 \mu\text{m}$$

⑥

* L: Const

* W ↑ 6 مرات

$$W_2 = 6 W_1$$

$$W_3 = 2 W_1$$

وهكذا في W_3

*** هنا ميفعل افقول $I_4 = I_3$ يبقى $W_3 = W_4$

لأن W_3 بتاعة NMOS ، W_4 بتاعة PMOS وكمات K_p و K_n متساويين

$$I_4 = \frac{1}{2} K_p \frac{W_4}{L} V_{ov_5}^2$$

$$20 \mu\text{A} = \frac{1}{2} (80 \mu\text{A}) \frac{W_4}{1} (0.2)^2$$

$$W_4 = 12.5 \mu\text{m}$$

$$\frac{I_5}{I_{ref}} = \frac{W_5/L}{W_4/L} \quad W_5 = W_4 * \frac{I_5}{I_4} = 12.5 * \frac{80}{20}$$

$$W_5 = 4 W_4 = 50 \mu\text{m}$$