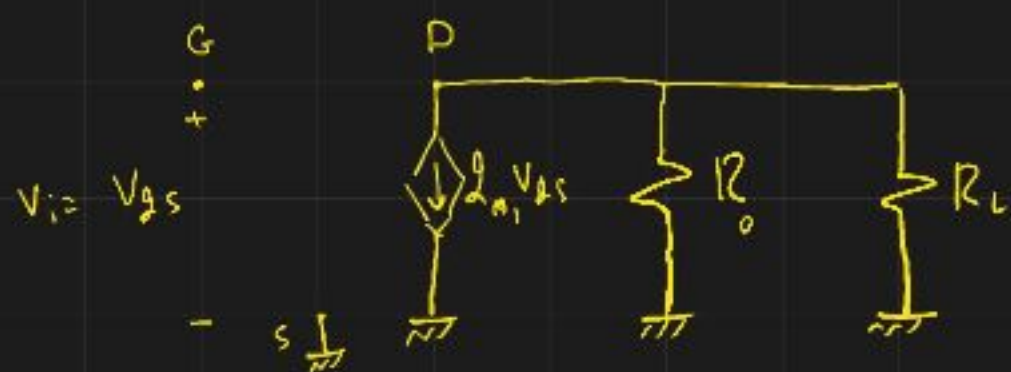


→ Remember CasCode amp with Load From Lec 9



$$\rightarrow R_o = R_o(Q_2) = g_{m2} r_{o2} R_s = g_{m2} r_{o2} r_{o1}$$


→  $R_L$  is the resistance at the drain of  $Q_2 \rightarrow$  which is  $r_{o3} \rightarrow \therefore R_L = r_{o3}$

$$\therefore A_v = -g_{m1} (R_o \parallel R_L)$$

$$\therefore A_v = -g_{m1} [ (g_{m2} r_{o2} r_{o1} \parallel r_{o3}) ]$$

\* CasCode differential amp:

→ half circuit (AC analysis):

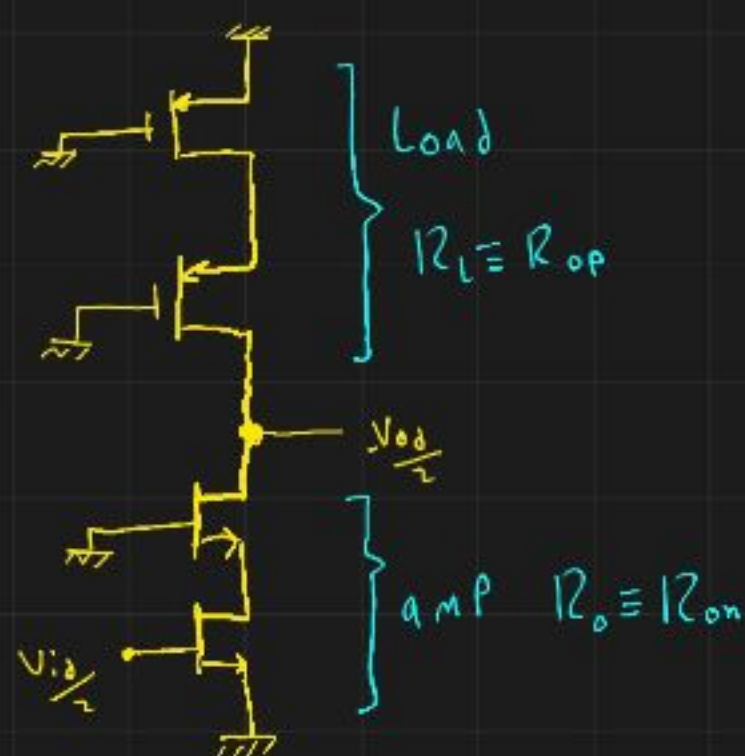

$$\rightarrow A_{v_d} = \frac{V_{od}}{V_{id}} = \frac{V_o}{V_{is}} = -g_m (R_{on} \parallel R_{op})$$


$$\bullet R_{on} = g_{m3} r_{o3} R_s = g_m r_{o3} r_{o1}$$

$$\bullet R_L = R_{op} = g_{m5} r_{o5} r_{o7}$$


$$\therefore A_{v_d} = \checkmark$$

\* CasCode Loaded with PMOS

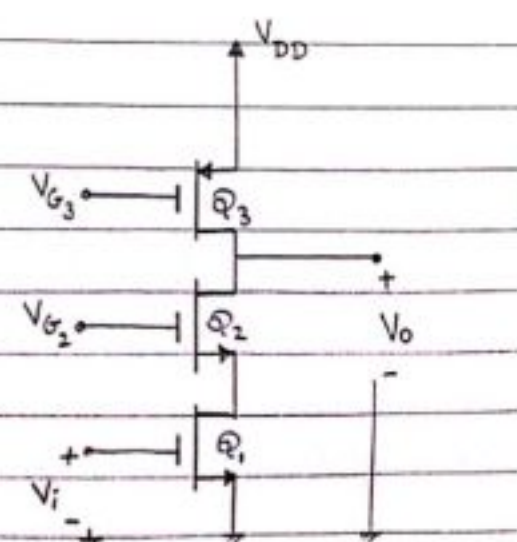$Q_1$ : Common Source  
 $Q_2$ : Common gate } CasCode  
 $Q_3$ : Load



\* CasCode differential amplifier

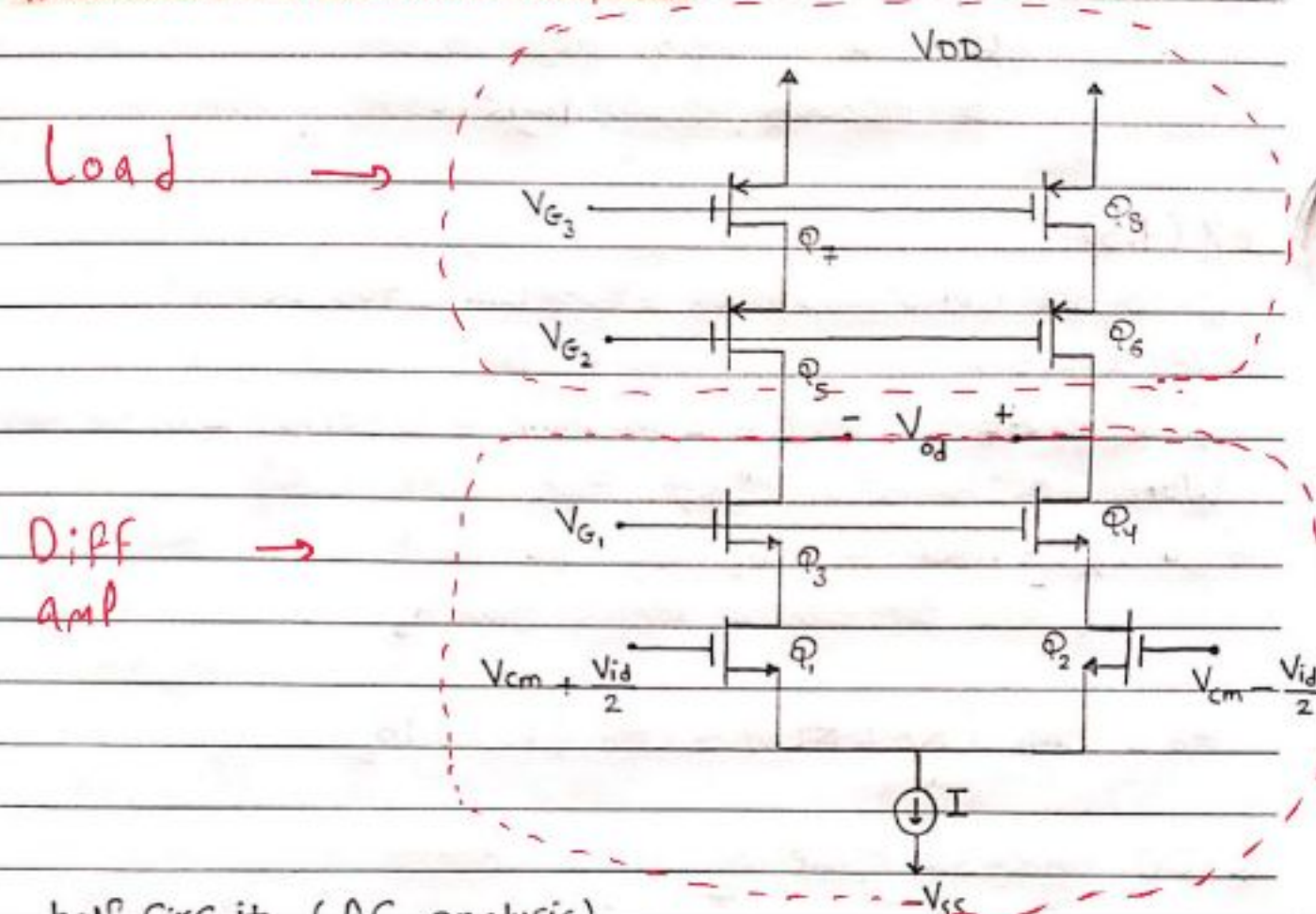




### EX (9.5)

0.18  $\mu\text{m}$  CMOS  $\mu_n C_{ox} = 4 \mu_p C_{ox} = 400 \mu\text{A/V}^2$   
 $|V_{t1}| = 0.5 \text{ V}$   $|V_A| = 10 \text{ V}/\mu\text{m}$   
 $I = 200 \mu\text{A}$   $L = 2 \text{ minimum} = 2(0.18) = 0.36 \mu\text{m}$   
 $|V_{ov}| = 0.2 \text{ V}$  "diff. Amp. with C.S"

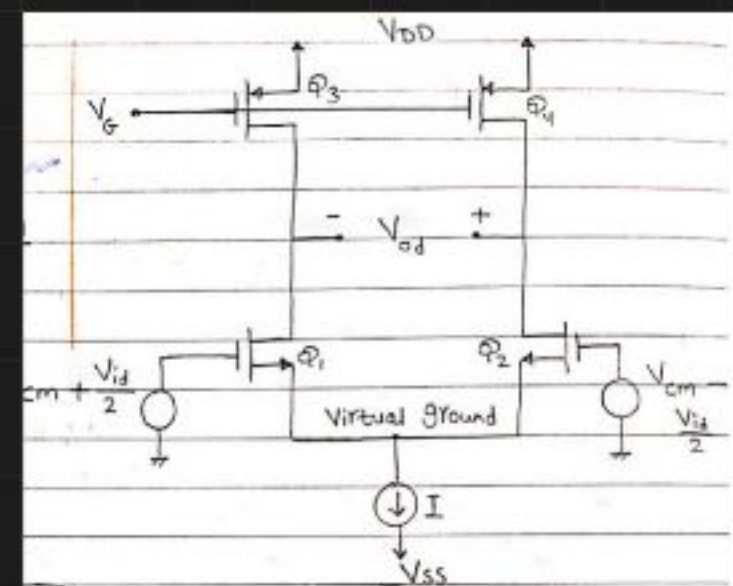find: \*  $\frac{W}{L}$  for  $Q_1, Q_2, Q_3, Q_4$   
 \* the differential voltage gain  $A_d$



$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{200}{2} = 100 \mu\text{A}$$

$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_1 (V_{ov})^2$$

$$100 \mu = \frac{1}{2} (400 \mu) \left(\frac{W}{L}\right)_1 (0.2)^2$$

$$\therefore \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 12.5$$

$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_3 (V_{ov})^2$$

$$100 \mu = \frac{1}{2} (100 \mu) \left(\frac{W}{L}\right)_3 (0.2)^2$$

$$\therefore \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 50$$

$$A_d = -g_m (r_{o1} \parallel r_{o3})$$

$$\rightarrow r_{o1} = \frac{V_A}{I_D} = \frac{V_A L}{I_D} = \frac{(10)(0.36)}{100 \mu} = 36 \text{ k}\Omega$$

$$\rightarrow r_{o3} = \frac{V_A}{I_D} = \frac{V_A L}{I_D} = \frac{(10)(0.36)}{100 \mu} = 36 \text{ k}\Omega$$

$$\rightarrow g_{m1} = \frac{2I_D}{V_{ov}} = \frac{I}{V_{ov}} = \frac{200 \mu}{0.2} = 1 \text{ mA/V}$$

$$\therefore A_d = -(1) \left(\frac{1}{2} \times 36\right) \rightarrow A_d = -18$$

### EX (9.6) CasCode diff. amplifier

$\mu_n C_{ox} = 4 \mu_p C_{ox} = 400 \mu\text{A/V}^2$   $|V_{t1}| = 0.5 \text{ V}$   
 $|V_A| = 10 \text{ V}/\mu\text{m}$   $I = 200 \mu\text{A}$   $L = 0.36 \mu\text{m}$   
 $|V_{ov}| = 0.2 \text{ V}$

find: ①  $\frac{W}{L}$  for each of  $Q_1 \rightarrow Q_8$  ②  $A_d$

$$I_{D1} = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_1 (V_{ov})^2$$

$$100 \mu = \frac{1}{2} (400 \mu) \left(\frac{W}{L}\right)_1 (0.2)^2$$

$$\therefore \left(\frac{W}{L}\right)_{1,2,3,4} = 12.5$$

$$I_{D5} = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_5 (V_{ov})^2$$

$$100 \mu = \frac{1}{2} (100 \mu) \left(\frac{W}{L}\right)_5 (0.2)^2$$

$$\therefore \left(\frac{W}{L}\right)_{5,6,7,8} = 50$$

$$A_d = -g_{m1} (R_{on} \parallel R_{op})$$

$$R_{on} = g_{m3} r_{o3} r_{o1}$$

$$R_{op} = g_{m5} r_{o5} r_{o7}$$


$$r_{o1} = \frac{V_A}{I_D} = \frac{V_A L}{I_D} = 36 \text{ k}\Omega$$

$$g_{m1} = \frac{2I_D}{V_{ov}} = \frac{I}{V_{ov}} = 1 \text{ mS}$$

$$\therefore R_{on} = 36^2 \text{ k}\Omega$$

$$\therefore R_{op} = 36^2 \text{ k}\Omega$$
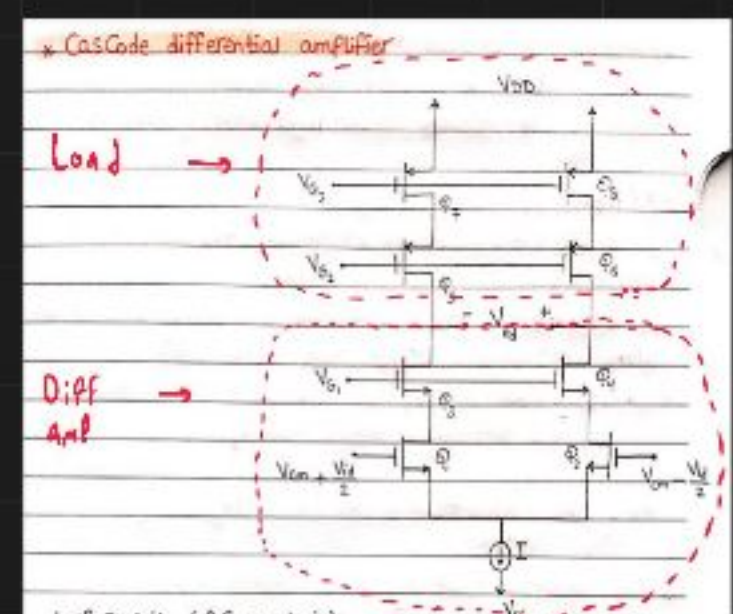
$$\therefore A_d = g_{m1} \frac{36^2}{2} = 648$$







# Prob. (9.20)

find the diff. half circuit, derive an expression for  $A_d$

$$A_d = \frac{V_{od}}{V_{id}} = f(g_m, R_D, R_S) \text{ , neglect early effect.}$$

1 → What is the gain  $R_S = 0 \rightarrow A_{dmax}$

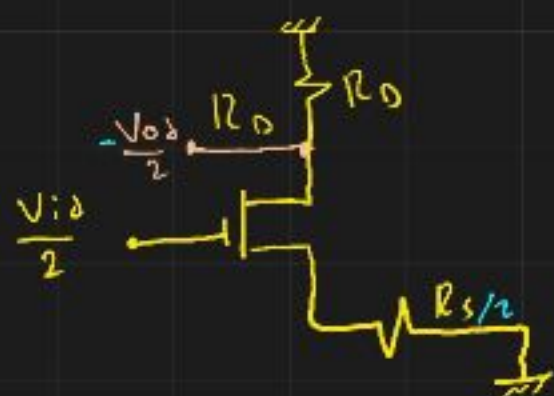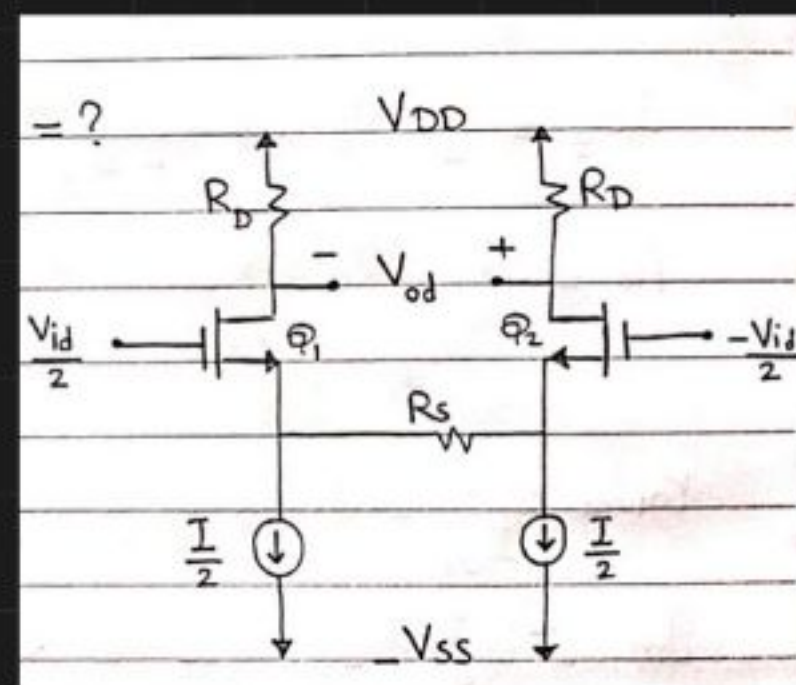2 → " " " Value of  $R_S$   $f(\frac{1}{g_m})$  that reduce gain to half value



→ at first glance ( $R_S$  usually very small)  $\rightarrow A_d = -g_m(R_D)$

→ Small signal model:

$$A_{Vd} = \frac{V_{od}}{V_{id}} = \frac{V_{od}/2}{V_{id}/2} = \frac{V_D}{V_G}$$

$$\rightarrow V_D = -g_m V_{GS} (R_D) \rightarrow \text{①} \quad , V_{GS} = V_G - V_S = \frac{V_{id}}{2} - V_S$$

$$\therefore V_D = -g_m \left( \frac{V_{id}}{2} - V_S \right) (R_D)$$

$$\therefore V_S = g_m V_{GS} R_S = g_m \left( \frac{V_{id}}{2} - V_S \right) R_S$$

$$\therefore V_S = g_m \frac{V_{id} R_S}{2} - g_m V_S R_S \rightarrow \therefore V_S (1 + g_m R_S) = g_m \frac{V_{id} R_S}{2} \rightarrow \therefore V_S = \frac{g_m \frac{V_{id} R_S}{2}}{1 + g_m R_S}$$

$$\therefore V_{GS} = V_G - V_S = \frac{V_{id}}{2} - \frac{g_m (V_{id}/2) R_S}{1 + g_m R_S} = \frac{V_{id} + V_{id} g_m R_S - V_{id} g_m R_S}{2(1 + g_m R_S)} = \frac{V_{id}/2}{1 + g_m R_S}$$

$$\therefore \text{①} \rightarrow V_D = -g_m \left( \frac{V_{id}/2}{1 + g_m R_S} \right) (R_D)$$

$$\therefore A_{Vd} = \frac{V_D}{V_{id}/2} \rightarrow \therefore A_{Vd} = -g_m \left( \frac{1}{1 + g_m R_S} \right) (R_D)$$

$$\rightarrow A_{dmax} \text{ @ } R_S = 0 \rightarrow A_{dmax} = -g_m (R_D)$$

→  $R_S$  when  $A_d = \frac{1}{2} A_{dmax}$

$$\hookrightarrow -g_m \left( \frac{1}{1 + g_m R_S} \right) (R_D) = -\frac{1}{2} g_m (R_D)$$

$$\therefore 1 + g_m \frac{R_S}{2} = 2$$

$$\therefore g_m \frac{R_S}{2} = 1$$

$$\therefore R_S = \frac{2}{g_m}$$

