


$r = \frac{V_-}{V_+}$ Reflection Coeff.

$Z_L = \frac{V_x}{I_x} \Big|_{x=0} = \frac{V_+ + V_-}{\frac{V_+}{Z_0} - \frac{V_-}{Z_0}} = Z_0 \frac{V_+ + V_-}{V_+ - V_-}$

$\therefore Z_L = Z_0 \frac{1 + V_-/V_+}{1 - V_-/V_+} = Z_0 \frac{1 + r}{1 - r}$

$\therefore r = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \therefore r = |r| e^{j\phi}$
Complex

$\therefore 0 \leq |r| \leq 1$
When $Z_L = Z_0$ "Perfect matching"

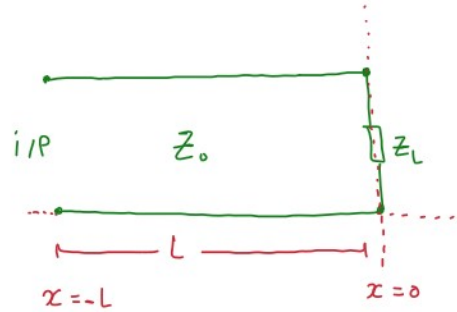

Input Impedance $Z_{i/p}$

$Z_{i/p} = \frac{V_x}{I_x} \Big|_{x=-L} = \frac{V_+ e^{j\gamma L} + V_- e^{-j\gamma L}}{\frac{V_+}{Z_0} e^{j\gamma L} - \frac{V_-}{Z_0} e^{-j\gamma L}}$
 $= Z_0 \frac{e^{j\gamma L} + \frac{V_-}{V_+} e^{-j\gamma L}}{e^{j\gamma L} - \frac{V_-}{V_+} e^{-j\gamma L}}$
 $= Z_0 \frac{e^{j\gamma L} + r e^{-j\gamma L}}{e^{j\gamma L} - r e^{-j\gamma L}}$
 $= Z_0 \frac{e^{j\gamma L} + (\frac{Z_L - Z_0}{Z_L + Z_0}) e^{-j\gamma L}}{e^{j\gamma L} - (\frac{Z_L - Z_0}{Z_L + Z_0}) e^{-j\gamma L}}$

$\therefore Z_{i/p} = Z_0 \frac{(Z_L + Z_0) e^{j\gamma L} + (Z_L - Z_0) e^{-j\gamma L}}{(Z_L + Z_0) e^{j\gamma L} - (Z_L - Z_0) e^{-j\gamma L}}$
 $= Z_0 \frac{Z_L (e^{j\gamma L} + e^{-j\gamma L}) + Z_0 (e^{j\gamma L} - e^{-j\gamma L})}{Z_0 (e^{j\gamma L} + e^{-j\gamma L}) + Z_L (e^{j\gamma L} - e^{-j\gamma L})}$
 $= Z_0 \frac{Z_L + Z_0 \left(\frac{e^{j\gamma L} - e^{-j\gamma L}}{e^{j\gamma L} + e^{-j\gamma L}} \right)}{Z_0 + Z_L \left(\frac{e^{j\gamma L} - e^{-j\gamma L}}{e^{j\gamma L} + e^{-j\gamma L}} \right)}$

$\therefore Z_{i/p} = Z_0 \frac{Z_L + Z_0 \tanh(\gamma L)}{Z_0 + Z_L \tanh(\gamma L)}$

General: Lossy T.L
Complex

→ For a lossless (ideal) T.L:

$Z_0 = R_0, \quad \gamma = j\beta, \quad \alpha = 0$

$\therefore \tanh(\gamma L) = \tanh(j\beta L) = j \tan(\beta L)$

$\therefore Z_{i/p} = R_0 \frac{Z_L + j R_0 \tan(\beta L)}{R_0 + j Z_L \tan(\beta L)}$ Still Complex

Short circuit Lossless T.L

$Z_L = 0$

x



Short Circuit Lossless T.L

$$Z_L = 0, Z_{in} = Z_{sc}$$

$$Z_{sc} = R_0 \frac{j R_0 \tan(\beta L)}{R_0} = j R_0 \tan(\beta L) = j X_{sc} \text{ "inductive"}$$

$$\therefore X_{sc} = R_0 \tan(\beta L)$$

$$\begin{aligned} \beta x &= \frac{\pi}{2} \\ \left(\frac{2\pi}{\lambda}\right)x &= \frac{\pi}{2} \\ x &= \frac{\lambda}{4} \end{aligned} \quad \left\{ \begin{aligned} \beta x &= \pi \\ \left(\frac{2\pi}{\lambda}\right)x &= \pi \\ x &= \frac{\lambda}{2} \end{aligned} \right.$$


Notes:

① if $L < \frac{\lambda}{4} \rightarrow$ the line becomes inductive \sim

② if $\frac{\lambda}{4} < L < \frac{\lambda}{2} \rightarrow$ capacitive \sim

③ if $L = \frac{\lambda}{4} \rightarrow$ Parallel Resonance L, C

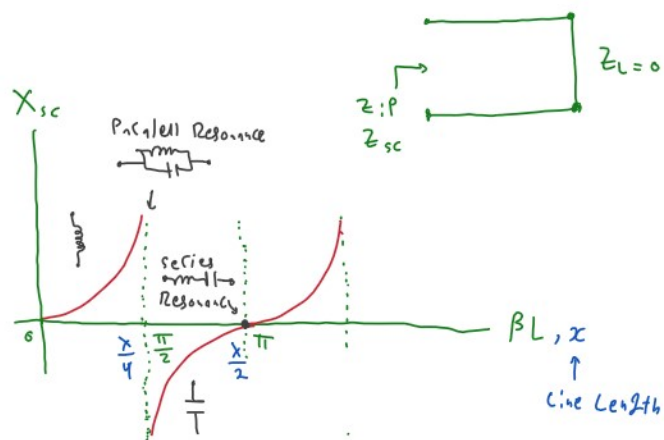④ $L = \frac{\lambda}{2} \rightarrow$ Series Resonance L, C




By changing the line length relative to signal wavelength we can control its behaviour.

Open Circuit Lossless T.L

$$\therefore Z_L = \infty$$

$$\therefore Z_{oc} = R_0 \frac{Z_L}{j Z_L \tan(\beta L)} = -j R_0 \cot(\beta L) = j X_{oc}$$

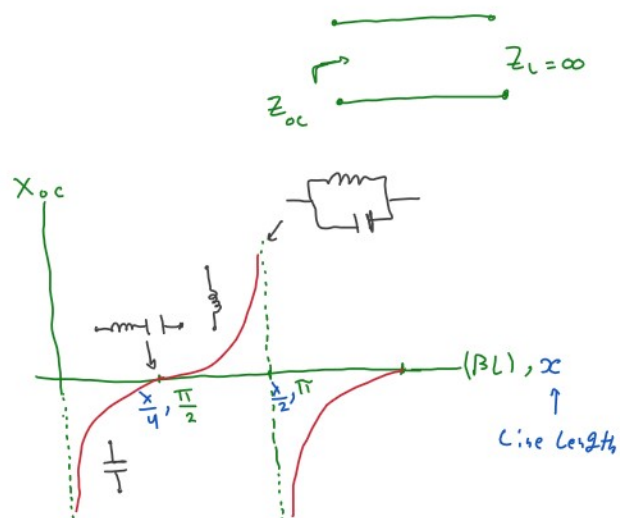
$$\therefore X_{oc} = -R_0 \cot(\beta L)$$



Voltage Standing Wave Ratio (VSWR)

$$\begin{aligned} VSWR &= \frac{V_{max}}{V_{min}} = \frac{|V_+| + |V_-|}{|V_+| - |V_-|} \\ &= \frac{1 + \frac{|V_-|}{|V_+|}}{1 - \frac{|V_-|}{|V_+|}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \end{aligned}$$

$$\therefore VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} \text{ "Real"}$$

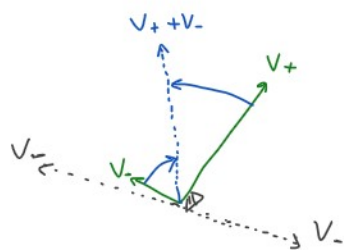

$$\therefore VSWR = \frac{1+|\Gamma|}{1-|\Gamma|} \quad \text{"real"}$$

$$0 \leq \Gamma \leq 1, \quad 1 < VSWR < \infty$$

$$\beta x_{\text{max-min}} = \frac{\pi}{2}$$

$$\therefore \left(\frac{2\pi}{\lambda} \right) x_{\text{max-min}} = \frac{\pi}{2}$$

$$\therefore x_{\text{max-min}} = \frac{\lambda}{4}$$

$$\left. \begin{array}{l} \therefore x_{\text{max-max}} = x_{\text{min-min}} = x_{\text{p-p}} = \lambda/2 \end{array} \right\}$$

