

Operation with a differential input voltage: (difference mode)

→ Current steers on branch only because $V_{G1}=0$ or $V_{G2}=0$

• If $V_{G2}=0$, $V_{G1}=V_i \rightarrow i_{D1}=I_D$, $i_{D2}=0$

$$I = \frac{1}{2} K'_n \left(\frac{W}{L}\right) (V_{GS1} - V_t)^2 \rightarrow V_{GS1} = V_t + \sqrt{\frac{2I}{K'_n \left(\frac{W}{L}\right)}}$$

→ From common mode: $\frac{I}{2} = \frac{1}{2} K'_n \left(\frac{W}{L}\right) (V_{OV})^2$

$$\therefore V_{OV} = \sqrt{\frac{I}{K'_n \left(\frac{W}{L}\right)}}$$

$$\therefore V_{GS1} = V_t + \sqrt{2} V_{OV}$$

Where V_{OV} is the overdrive voltage corresponding to a current of $\frac{I}{2}$

$$\therefore V_{iD} = V_{GS1} + V_s$$

$$\therefore i_{D2}=0 \rightarrow \text{Cutoff} \therefore V_{GS2} = V_t \rightarrow V_{G2} - V_{S2} = V_t \rightarrow V_{S1} = V_{S2} \rightarrow V_{S1} = V_{S2} = -V_t$$

$$\therefore V_{iD} = V_t + \sqrt{2} V_{OV} \rightarrow V_t$$

$$\therefore V_{iD} = \sqrt{2} V_{OV}$$

→ $V_{iD} > V_{iD_{max}}$ will cause all current to steer towards one branch.

So for small differential signal: $|V_{iD}| < \sqrt{2} V_{OV}$

$$-\sqrt{2} V_{OV} \leq V_{iD} \leq \sqrt{2} V_{OV}$$

$$V_{GS2} > V_{GS1}$$

$$\rightarrow i_{D2} = I, i_{D1} = 0$$

$$V_{GS1} > V_{GS2}$$

$$\rightarrow i_{D1} = I, i_{D2} = 0$$

Large signal operation:

→ $|V_{iD}| > \sqrt{2} V_{OV}$, taking into consideration that

$$V_{iD} = V_{GS1} - V_{GS2} = V_{G1} - V_{G2}, \text{ and } i_{D1} + i_{D2} = I_D$$




→ We can get the following expression:

$$i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}}\right) \left(\frac{V_{iD}}{2}\right) \sqrt{1 - \left(\frac{V_{iD}}{2V_{OV}}\right)^2}$$

$$i_{D2} = \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \left(\frac{V_{iD}}{2}\right) \sqrt{1 - \left(\frac{V_{iD}}{2V_{OV}}\right)^2}$$

→ normalized plot of current (i_{D1}, i_{D2}) vs V_{iD} :

Region where linear amp is possible

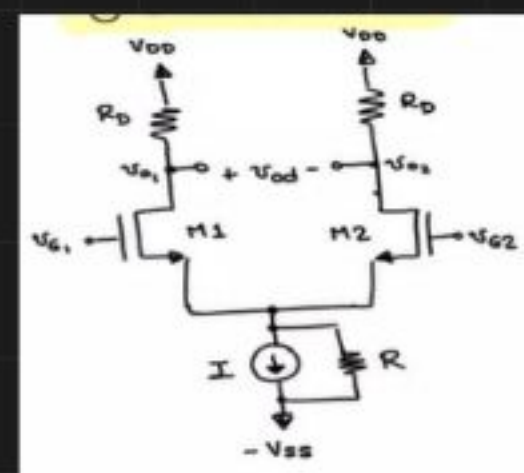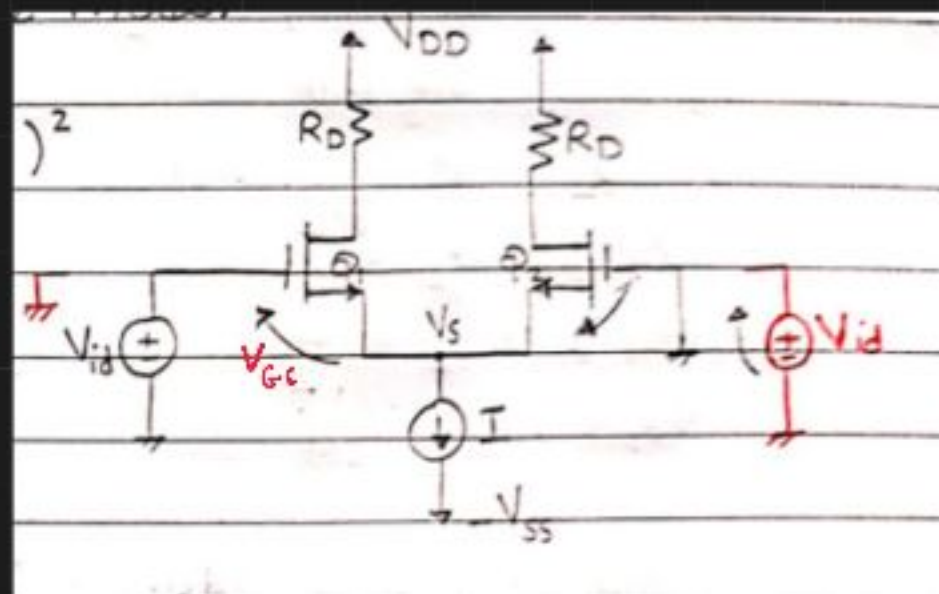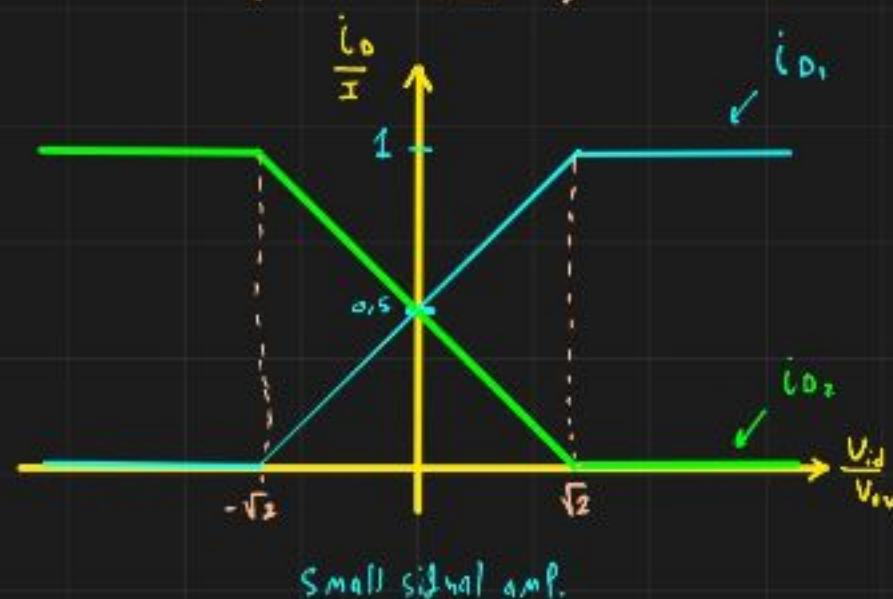

★ Small signal operations:

$$\rightarrow V_{id} < \sqrt{2} V_{ov}, \quad V_{id} \ll V_{ov}$$

$$\therefore \frac{V_{id}}{2V_{ov}} \ll 1$$

$$\cdot i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{ov}}\right) \left(\frac{V_{id}}{2}\right) \sqrt{1 - \left(\frac{V_{id}}{2V_{ov}}\right)^2}$$

$$\rightarrow \therefore i_{D1} = \frac{I}{2} + \underbrace{\left(\frac{I}{V_{ov}}\right) \left(\frac{V_{id}}{2}\right)}_{i_d}$$

$$\cdot i_{D2} = \frac{I}{2} - \left(\frac{I}{V_{ov}}\right) \left(\frac{V_{id}}{2}\right) \sqrt{1 - \left(\frac{V_{id}}{2V_{ov}}\right)^2}$$

$$\rightarrow \therefore i_{D2} = \frac{I}{2} - \left(\frac{I}{V_{ov}}\right) \left(\frac{V_{id}}{2}\right)$$

Large signal Small signal

$$\cdot i_d = \left(\frac{I}{V_{ov}}\right) \left(\frac{V_{id}}{2}\right) \quad \therefore g_m = \frac{2I_D}{V_{ov}} = \frac{I}{V_{ov}}$$

DC component Component

$$\therefore i_d = g_m \left(\frac{V_{id}}{2}\right)$$

→ Notes:

1). increasing V_{ov} extends the Linear range ($-\sqrt{2} V_{ov} < V_{id} < \sqrt{2} V_{ov}$)

+ tradeoff: decrease in gain (g_m) $\rightarrow g_m = \frac{2I_D}{V_{ov}}$

2) decrease V_{ov} gain \uparrow but Linear region \downarrow

3) We can increase I (bias current) to increase gain

+ tradeoff: higher power dissipation.

$$\rightarrow V_{G1} = V_{cm} + \frac{V_{id}}{2}$$

$$\rightarrow V_{G2} = V_{cm} - \frac{V_{id}}{2}$$

$$\rightarrow i_{D1} = \frac{I}{2} + g_m \left(\frac{V_{id}}{2}\right)$$

$$\rightarrow i_{D2} = \frac{I}{2} - g_m \left(\frac{V_{id}}{2}\right)$$

$$\therefore V_{D1} = \left(V_{DD} - \frac{I}{2} R_D\right) - g_m \left(\frac{V_{id}}{2}\right) R_D$$




$$\therefore V_{D2} = \left(V_{DD} - \frac{I}{2} R_D\right) + g_m \left(\frac{V_{id}}{2}\right) R_D$$

DC

AC

$$\rightarrow A_d = \frac{V_{od}}{V_{id}} = \frac{V_{od1} - V_{od2}}{V_{id}} = \frac{-g_m V_{id} R_D}{V_{id}}$$
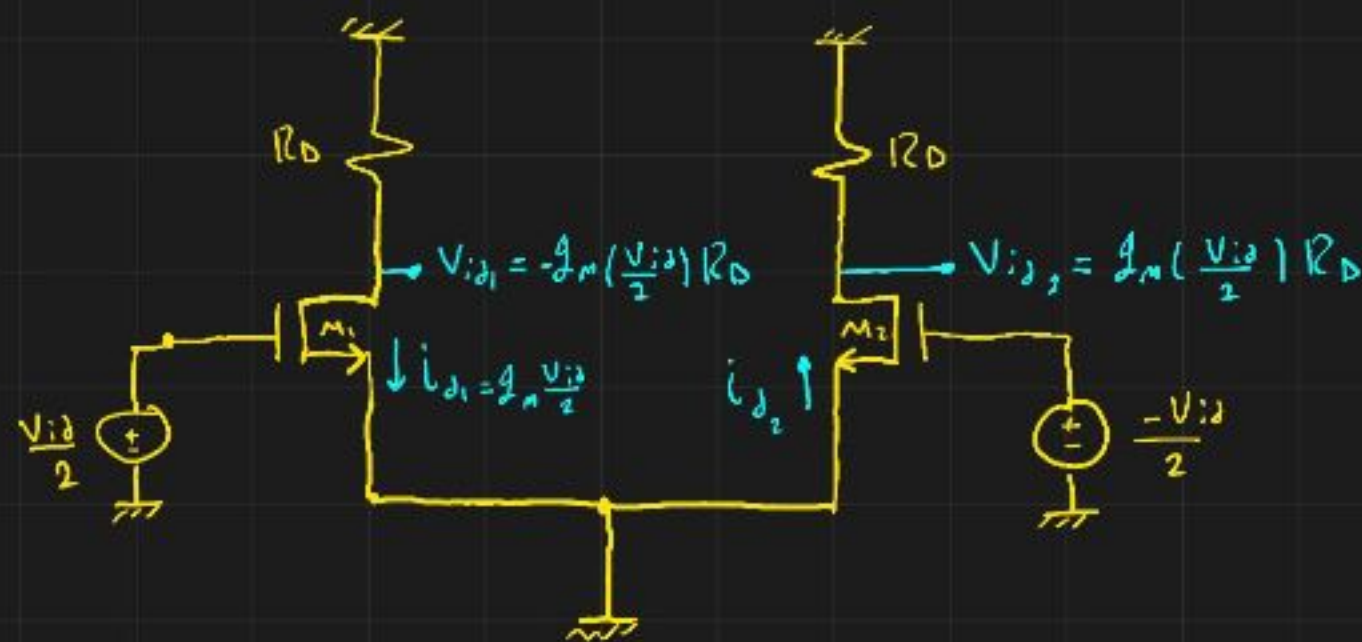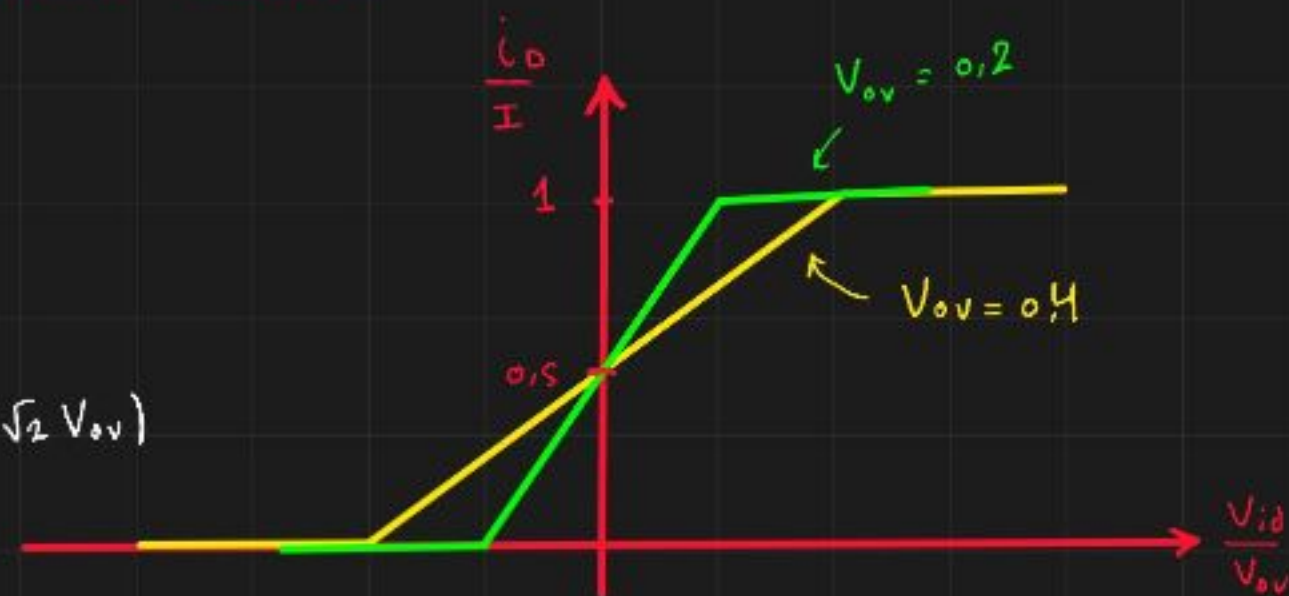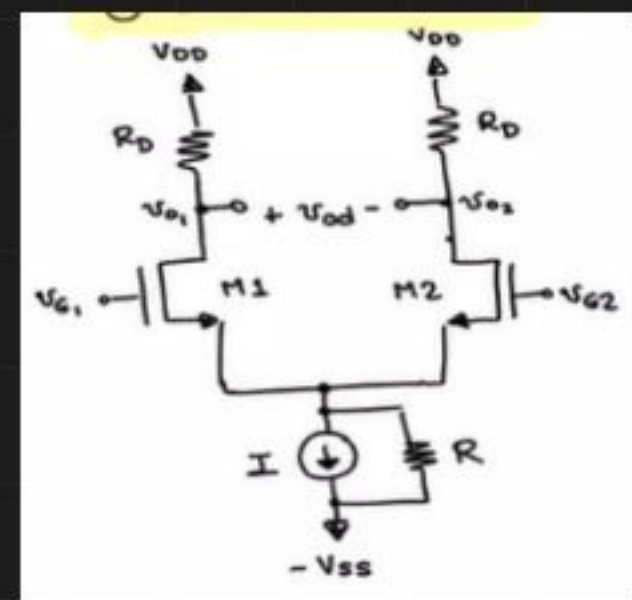
$$\rightarrow \therefore A_d = -g_m R_D$$



AC equivalent circuit:

$$V_{od} = V_{d1} - V_{d2}$$

$$\rightarrow V_{d1} = -g_m V_{gs1} R_D = -g_m \frac{V_{id}}{2} R_D$$

$$\rightarrow V_{d2} = -g_m V_{gs2} R_D = g_m \frac{V_{id}}{2} R_D$$




$$\therefore V_{od} = -g_m V_{id} R_D$$

$$\therefore A_{vd} = \frac{V_{od}}{V_{id}} \rightarrow \therefore A_{vd} = -g_m R_D$$

→ diff. amp. cancels noise because it's applied to both terminals.

→ gain of diff. amp = 2 gain of each trans.

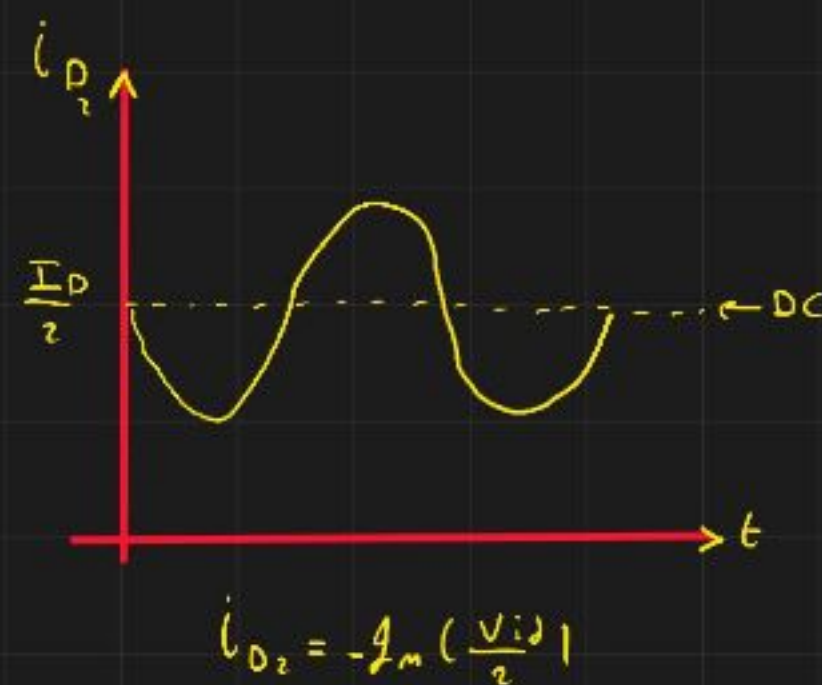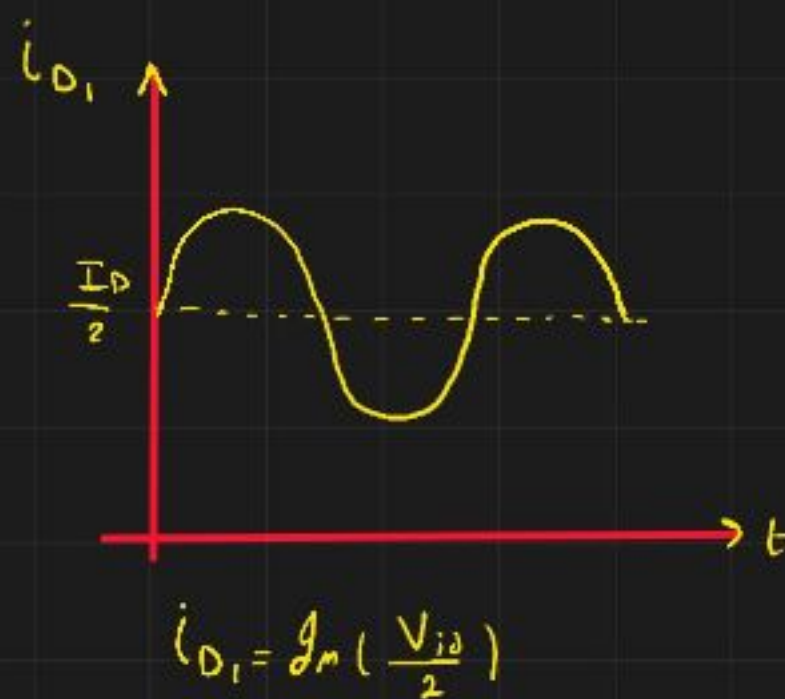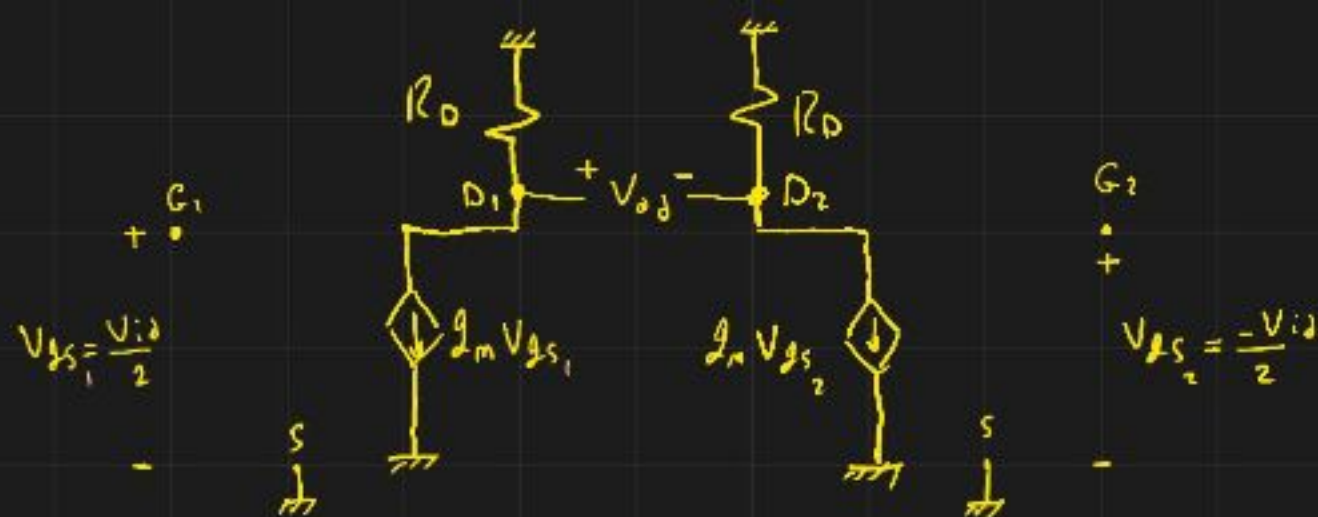→ note that the o/p at D_1 will be flipped ($V_{d1} = -g_m V_{gs1} R_D$)





$$i_{D1} + i_{D2} = I, g_m = \frac{I}{V_{ov}}$$

Ex (9.2) Page (621)

→ get diff voltage gain $A_d = ?$

→ AC analysis (half circuit):

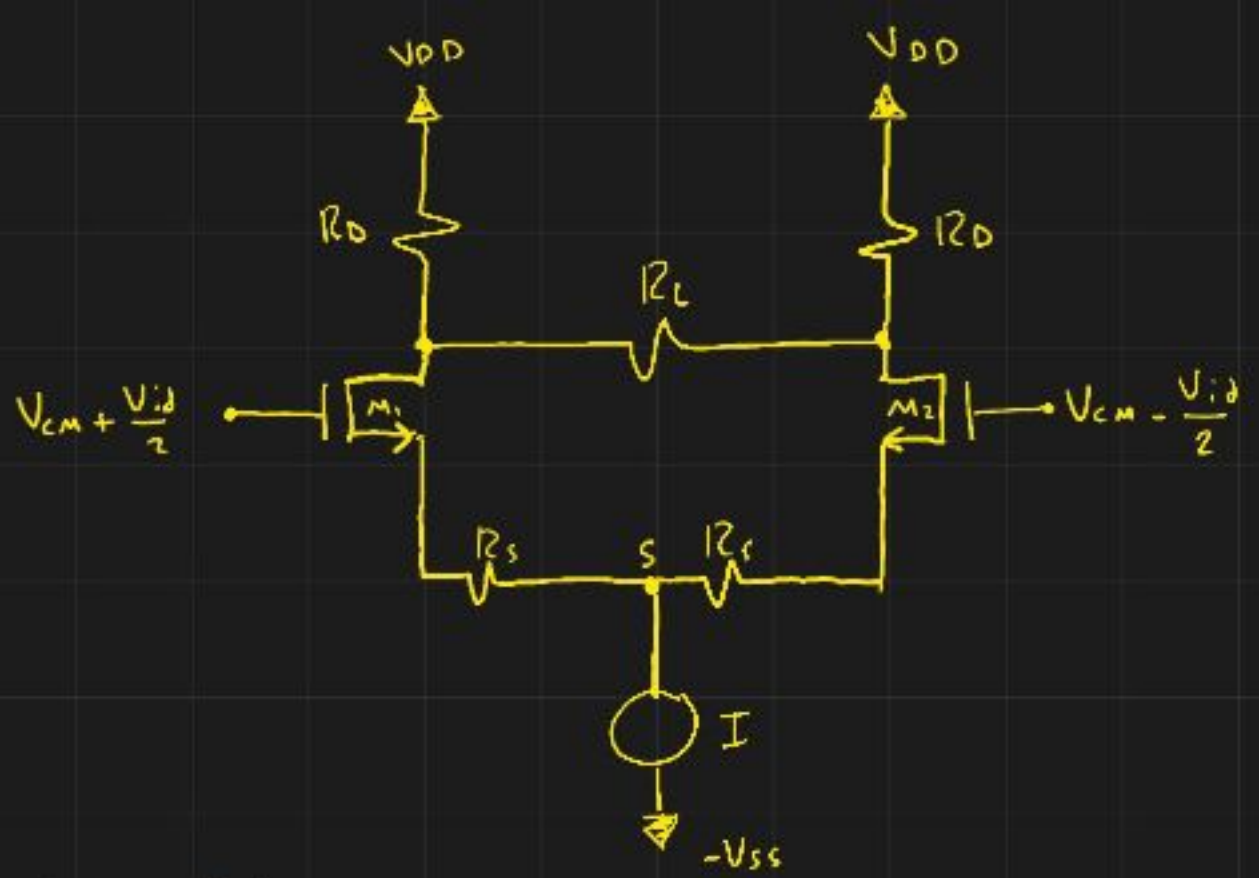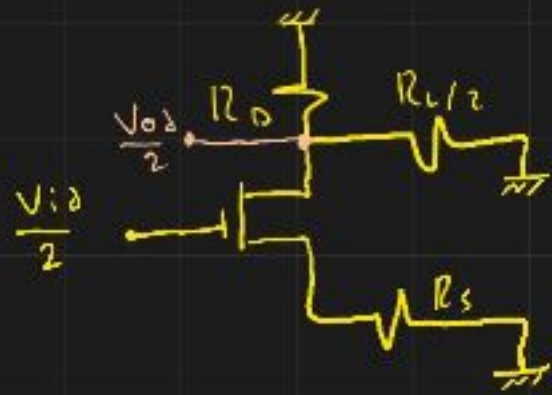

→ at first glance (R_S usually very small) $\rightarrow A_d = -g_m (R_D \parallel \frac{R_L}{2})$

→ Small signal model:

$$A_{v_d} = \frac{v_{od}}{v_{id}} = \frac{v_{od/2}}{v_{id/2}} = \frac{v_D}{v_G}$$

$$\rightarrow v_D = -g_m v_{GS} (R_D \parallel \frac{R_L}{2}) \rightarrow \textcircled{1} \quad , \quad v_{GS} = v_G - v_S = \frac{v_{id}}{2} - v_S$$

$$\therefore v_D = -g_m (\frac{v_{id}}{2} - v_S) (R_D \parallel \frac{R_L}{2})$$


$$\therefore v_S = g_m v_{GS} R_S = g_m (\frac{v_{id}}{2} - v_S) R_S$$

$$\therefore v_S = g_m \frac{v_{id}}{2} R_S - g_m v_S R_S \rightarrow \therefore v_S (1 + g_m R_S) = g_m \frac{v_{id}}{2} R_S \rightarrow \therefore v_S = \frac{g_m \frac{v_{id}}{2} R_S}{1 + g_m R_S}$$

$$\therefore v_{GS} = v_G - v_S = \frac{v_{id}}{2} - \frac{g_m (\frac{v_{id}}{2}) R_S}{1 + g_m R_S} = \frac{v_{id} + \cancel{v_{id} g_m R_S} - \cancel{v_{id} g_m R_S}}{2(1 + g_m R_S)} = \frac{v_{id}/2}{1 + g_m R_S}$$


$$\therefore \textcircled{1} \rightarrow v_D = -g_m \left(\frac{v_{id}/2}{1 + g_m R_S} \right) (R_D \parallel \frac{R_L}{2})$$
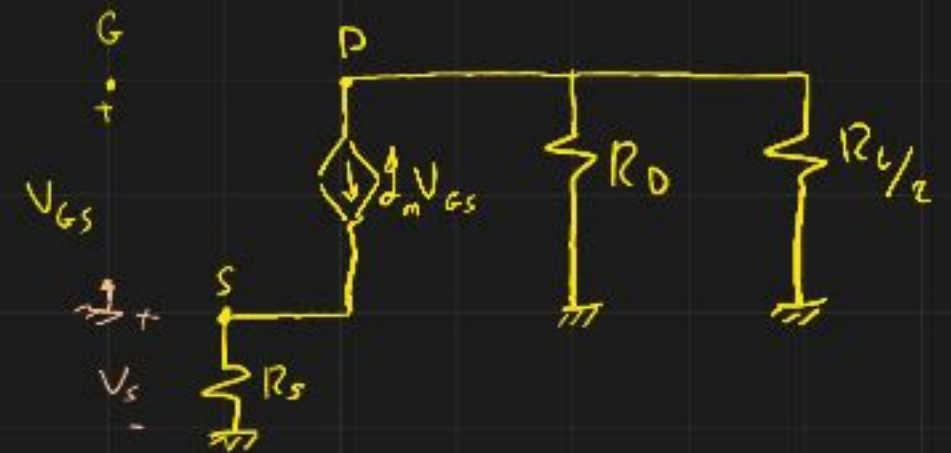
$$\therefore A_{v_d} = \frac{v_D}{v_{id}/2} \rightarrow \therefore A_{v_d} = -g_m \left(\frac{1}{1 + g_m R_S} \right) (R_D \parallel \frac{R_L}{2})$$





* The differential amplifier with Current source Loads
Page(622)

get $A_d = \frac{V_{od}}{V_{id}}$

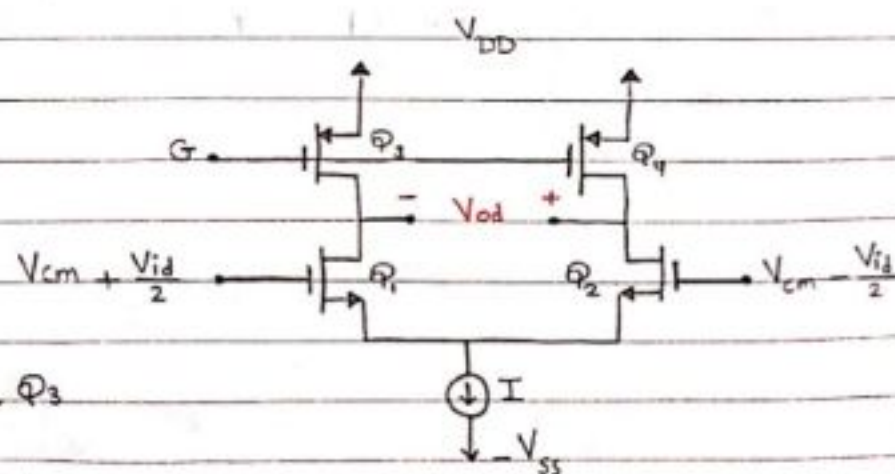

V_G عن طريق Q_1, Q_3

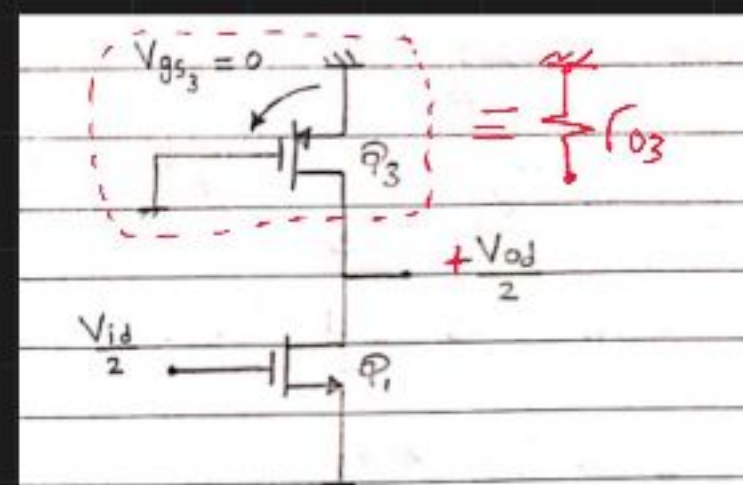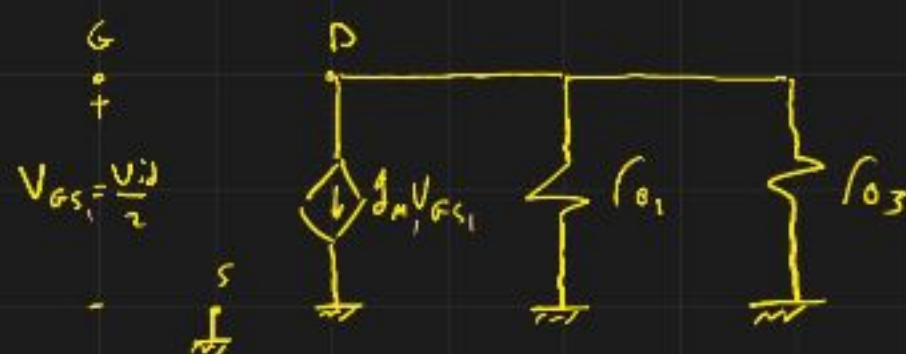→ AC analysis (half circuit) → Q_3 is considered a load and its o/p resistance is r_{o3}
So in the small signal model Q_3, Q_4 will be related by r_{o3}, r_{o4}



$$\rightarrow A_{V_d} = \frac{V_{od}}{V_{id}} = \frac{V_{od}/2}{V_{id}/2} = \frac{V_D}{V_{GS}}$$

$$\rightarrow V_D = -g_{m1} V_{GS1} (r_{o1} \parallel r_{o3})$$

$$\rightarrow \therefore A_{V_d} = -g_{m1} (r_{o1} \parallel r_{o3})$$