
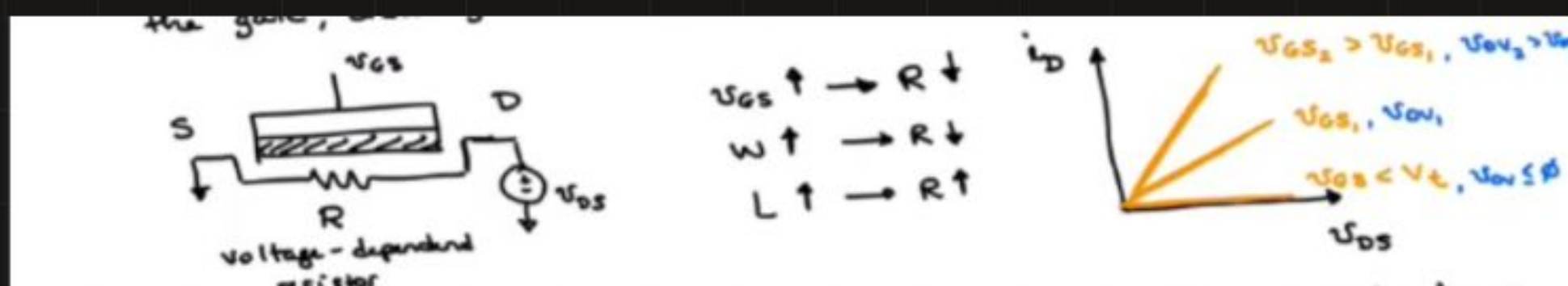


★ Principle of operation:

→ Gate Voltage (input) controls drain-to-source current (output) i_D or i_O

1) For $V_{GS} = 0$, no current flows ($i_D = 0$) → transistor is off.

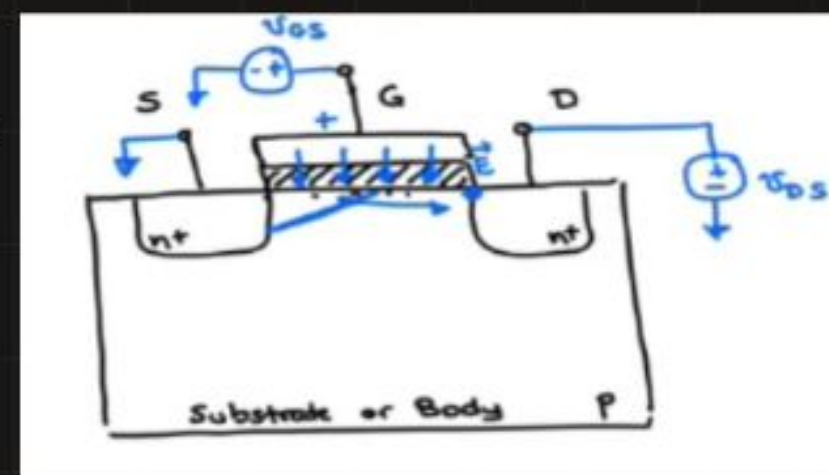2) as V_{GS} increases, electrons are attracted towards the region underneath the gate, filling available holes and creating an **inversion layer** underneath the gate, creating a resistive path between drain and source.



• V_t : threshold voltage → min voltage V_{GS} needed to create an inversion layer "channel"

• V_{ov} : overdrive voltage → amount of voltage applied at the gate in excess of V_t ($V_{ov} = V_{GS} - V_t$)


→ $V_t > 0$ for nMOS, $V_t < 0$ for PMOS, typically $|V_t| \leq 1\text{V}$

3) as $V_{DS} \uparrow$ the $i_D \uparrow$ until reaching a certain max V_{DS} for current V_{GS} , after this point the transistor enters the saturation region → i_D is constant for further increase in V_{DS} .


this is due to "Channel Pinch-off"

→ for linear amplification will use transistor in saturation region.

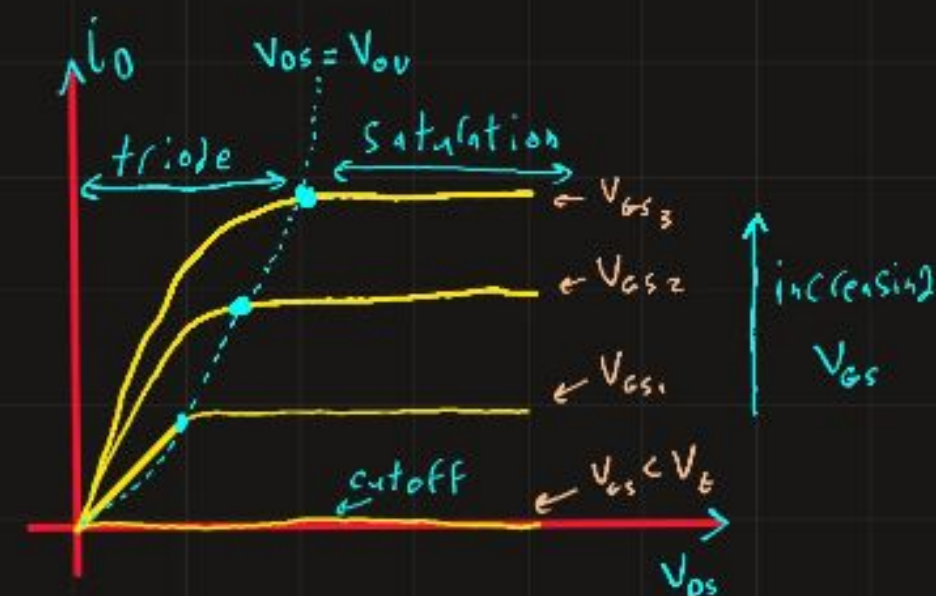as i_D increases linearly with increasing V_{GS} in saturation region.




IV characteristics:

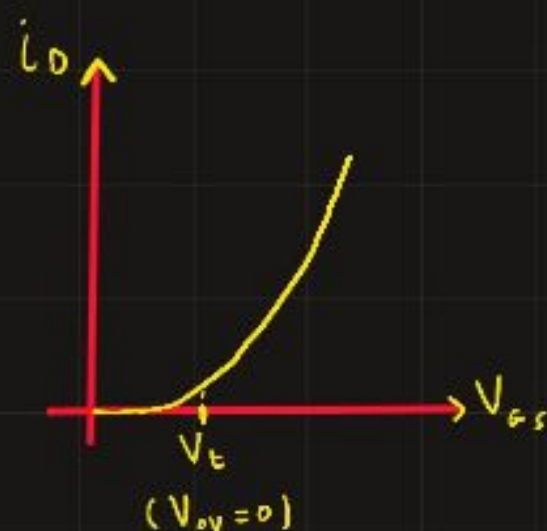

→ $V_{GS} < V_t \rightarrow$ no channel \rightarrow cutoff $\rightarrow I_D = 0$

→ $V_{GS} > V_t \rightarrow$ a channel is induced

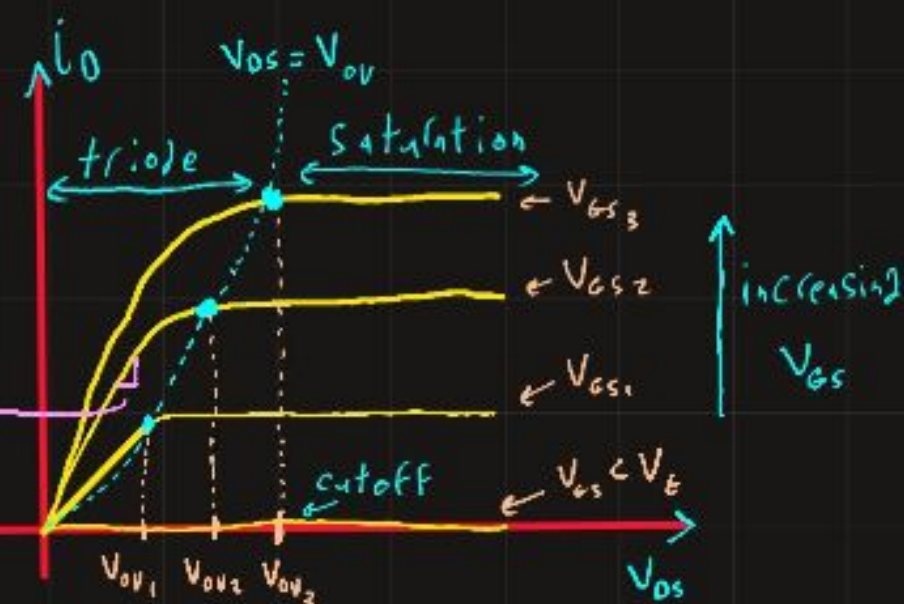→ $V_{DS} < V_{OV}$: triode region \rightarrow Voltage Controlled Resistor $\rightarrow I_D(V_{GS}, V_{DS})$
 → $V_{DS} > V_{OV}$: Saturation region \rightarrow Voltage-Controlled Current Source



trans conductance device $\rightarrow I_D \propto V_{GS}$

$$I_D = \frac{1}{2} K_n (V_{GS} - V_t)^2$$

Channel Length Modulation:


→ in Saturation region we drew the function as constant, meaning " I_D doesn't increase as V_{DS} increases" " I_D indep. of V_{DS} "
 this isn't true, there will be a small change in I_D as V_{DS} changes due to internal resistance between source-drain.

→ to account this change we use λ .

$$I_D = \frac{1}{2} K_n (V_{GS} - V_t)^2$$


λ : channel-length modulation parameter (V^{-1})
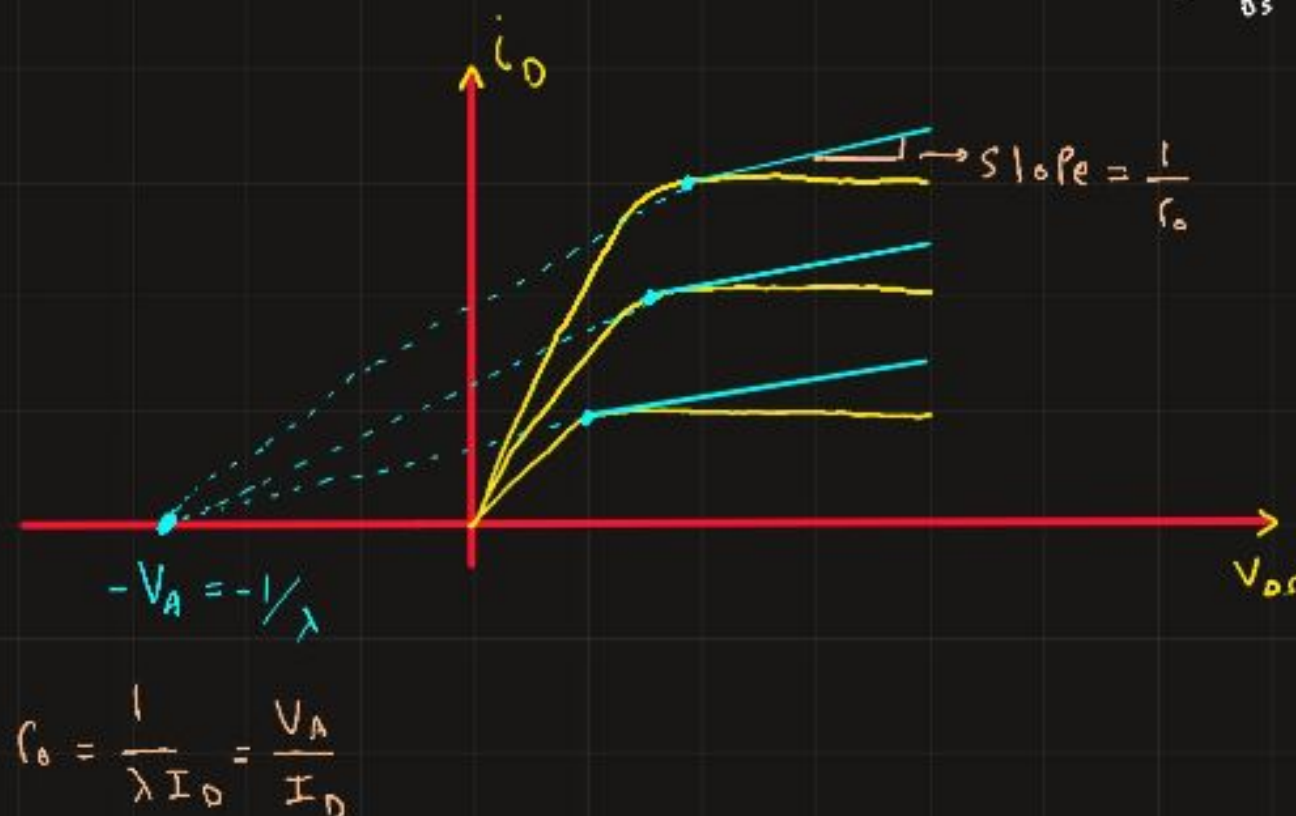
$$\rightarrow I_D = \frac{1}{2} K_n (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$



* Mosfet as amplifier:

- used in Saturation region ($I_D = K_n V_{GS}^2$) \rightarrow Small changes in V_{GS} results in large changes in I_D .
- first we set the Q-point in the preferred region at the middle of the saturation region to avoid entering the triode region.
- Q-point is set using DC biasing circuit (V_{GS}, I_D)
- the changes in I_D results in changing in V_{DS} .
- All the changes (V_{GS}, I_D, V_{DS}) is around the Q-point.

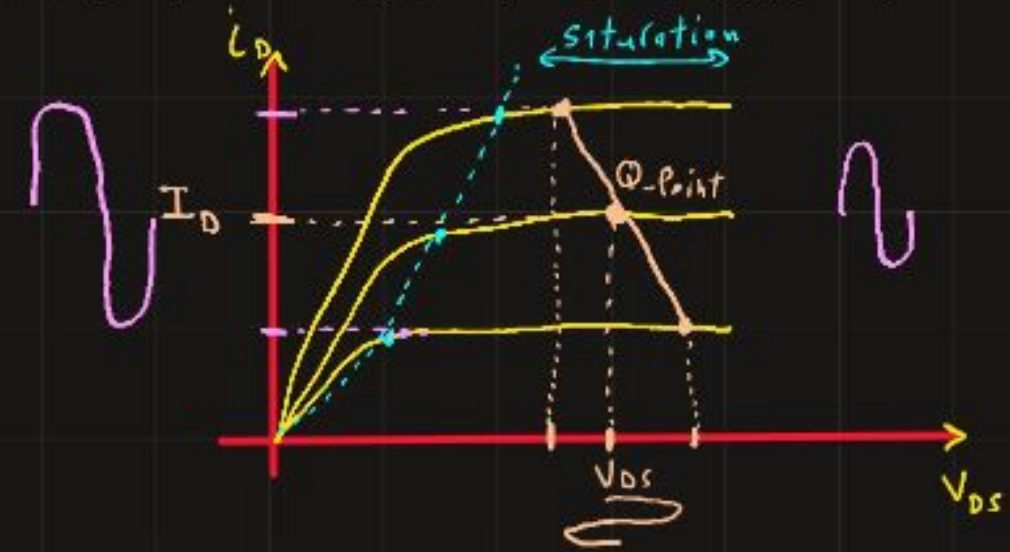

* DC Analysis example:

Find Q-point (V_{GS}, I_D, V_{DS})

\rightarrow Assume M1 in Saturation.

$$V_G = \frac{100}{100+100} (10) = 5V$$

$$I_D = \frac{1}{2} K_n (V_{GS} - V_t)^2$$

$$V_{GS} = V_G - V_S = 5 - 6 I_D$$

$$\therefore I_D = \frac{1}{2} (5 - 6 I_D - 1)^2 \rightarrow \therefore I_D = 0.89 \text{ mA}, I_D = 0.5 \text{ mA}$$

• First solution: $I_D = 0.89 \text{ mA}$

$$\rightarrow V_S = 6 I_D = 5.34V$$

$$\rightarrow V_{GS} = 5 - 5.34 = -0.34 \therefore \text{rejected } V_{GS} < 0$$

$$V_{DS} = V_D - V_S = 10 - 6(0.5) - 6(0.5)$$

$$\therefore V_{DS} = 4V$$


$$V_{DS} > V_{GS} - V_t \quad \text{Saturation}$$

$$4 > 2 - 1$$

• Second solution: $I_D = 0.5 \text{ mA}$


$$\rightarrow V_S = 6 I_D = 3V$$
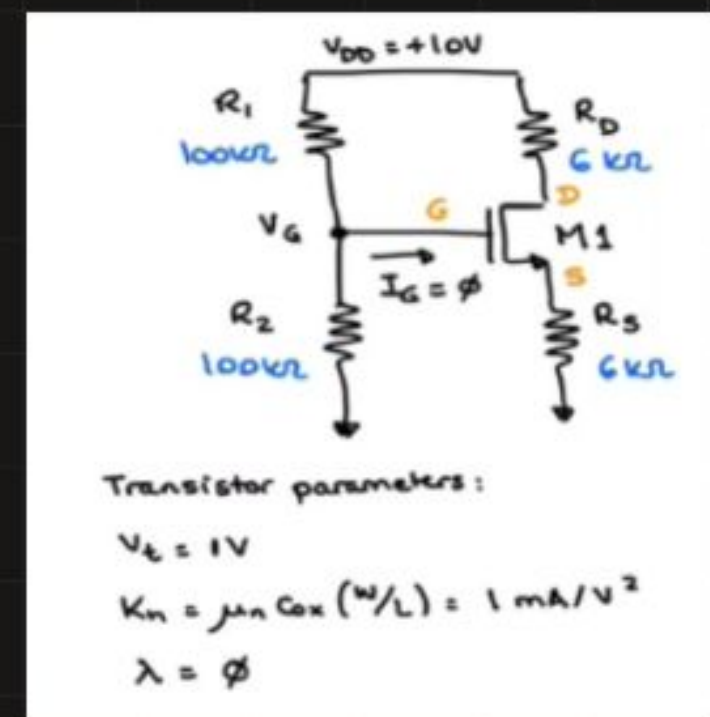
$$\rightarrow \therefore V_{GS} = 5 - 3 = 2 \therefore \text{accepted}$$



★ Small Signal Model:

Hybrid- π model

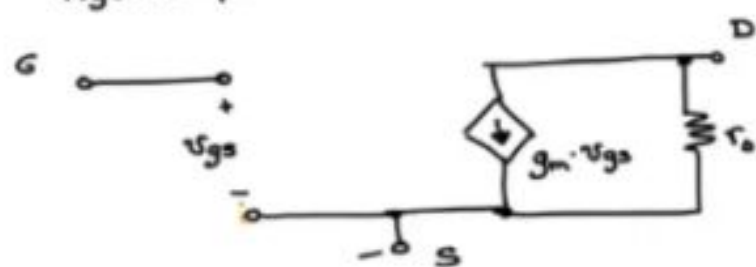

$$i_D = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) (v_{GS} - V_t)^2 = \frac{1}{2} K_n \cdot v_{ov}^2$$

$$g_m = \frac{\partial i_D}{\partial v_{GS}} = K_n \cdot v_{ov} = \frac{2 I_D}{v_{ov}} = \sqrt{2 K_n \cdot I_D}$$

Therefore,

$$\begin{aligned}
 g_m &= (\mu_n C_{ox}) \left(\frac{W}{L} \right) (v_{GS} - V_t) && \leftarrow \text{no } I_D \\
 &= \frac{2 I_D}{v_{GS} - V_t} && \leftarrow \text{no process parameters (no } K_n) \\
 &= \sqrt{(\mu_n C_{ox}) \left(\frac{W}{L} \right) I_D} && \leftarrow \text{no } v_{GS} \text{ (no } v_{ov})
 \end{aligned}$$

Taking into account channel-length modulation (i.e., finite r_o):

$$i_D = \frac{1}{2} K_n v_{ov}^2 (1 + \lambda \cdot v_{DS}) \quad \lambda = \frac{1}{V_A}$$

$$r_o = \left[\frac{\partial i_D}{\partial v_{DS}} \right]^{-1} = [\lambda \cdot I_D]^{-1} = \frac{1}{\lambda \cdot I_D} = \boxed{\frac{|V_A|}{I_D}}$$